12

Boolean Algebra

- 12.1 Boolean Functions
- 12.2 Representing Boolean Functions
- 12.3 Logic Gates
- **12.4** Minimization of Circuits

he circuits in computers and other electronic devices have inputs, each of which is either a 0 or a 1, and produce outputs that are also 0s and 1s. Circuits can be constructed using any basic element that has two different states. Such elements include switches that can be in either the on or the off position and optical devices that can be either lit or unlit. In 1938 Claude Shannon showed how the basic rules of logic, first given by George Boole in 1854 in his The Laws of Thought, could be used to design circuits. These rules form the basis for Boolean algebra. In this chapter we develop the basic properties of Boolean algebra. The operation of a circuit is defined by a Boolean function that specifies the value of an output for each set of inputs. The first step in constructing a circuit is to represent its Boolean function by an expression built up using the basic operations of Boolean algebra. We will provide an algorithm for producing such expressions. The expression that we obtain may contain many more operations than are necessary to represent the function. Later in the chapter we will describe methods for finding an expression with the minimum number of sums and products that represents a Boolean function. The procedures that we will develop, Karnaugh maps and the Quine–McCluskey method, are important in the design of efficient circuits.

12.1

Boolean Functions

12.1.1 Introduction

Boolean algebra provides the operations and the rules for working with the set $\{0, 1\}$. Electronic and optical switches can be studied using this set and the rules of Boolean algebra. The three operations in Boolean algebra that we will use most are complementation, the Boolean sum, and the Boolean product. The **complement** of an element, denoted with a bar, is defined by $\overline{0} = 1$ and $\overline{1} = 0$. The Boolean sum, denoted by + or by OR, has the following values:

$$1+1=1$$
, $1+0=1$, $0+1=1$, $0+0=0$.

The Boolean product, denoted by \cdot or by AND, has the following values:

$$1 \cdot 1 = 1$$
, $1 \cdot 0 = 0$, $0 \cdot 1 = 0$, $0 \cdot 0 = 0$.

When there is no danger of confusion, the symbol · can be deleted, just as in writing algebraic products. Unless parentheses are used, the rules of precedence for Boolean operators are: first, all complements are computed, followed by all Boolean products, followed by all Boolean sums. This is illustrated in Example 1.

EXAMPLE 1 Find the value of $1 \cdot 0 + \overline{(0+1)}$.

Solution: Using the definitions of complementation, the Boolean sum, and the Boolean product, it follows that

$$1 \cdot 0 + \overline{(0+1)} = 0 + \overline{1} \\ = 0 + 0 \\ = 0.$$

The complement, Boolean sum, and Boolean product correspond to the logical operators, \neg , \lor , and \land , respectively, where 0 corresponds to \mathbf{F} (false) and 1 corresponds to \mathbf{T} (true). Equalities in Boolean algebra can be directly translated into equivalences of compound propositions. Conversely, equivalences of compound propositions can be translated into equalities in Boolean algebra. We will see later in this section why these translations yield valid logical equivalences and identities in Boolean algebra. Example 2 illustrates the translation from Boolean algebra to propositional logic.

EXAMPLE 2 Translate $1 \cdot 0 + \overline{(0+1)} = 0$, the equality found in Example 1, into a logical equivalence.

Solution: We obtain a logical equivalence when we translate each 1 into a **T**, each 0 into an **F**, each Boolean sum into a disjunction, each Boolean product into a conjunction, and each complementation into a negation. We obtain

$$(T \wedge F) \vee \neg (T \vee F) \equiv F.$$

Example 3 illustrates the translation from propositional logic to Boolean algebra.

EXAMPLE 3 Translate the logical equivalence $(T \land T) \lor \neg F \equiv T$ into an identity in Boolean algebra.

Solution: We obtain an identity in Boolean algebra when we translate each **T** into a 1, each **F** into a 0, each disjunction into a Boolean sum, each conjunction into a Boolean product, and each negation into a complementation. We obtain

$$(1\cdot 1) + \overline{0} = 1.$$

12.1.2 Boolean Expressions and Boolean Functions

Let $B = \{0, 1\}$. Then $B^n = \{(x_1, x_2, ..., x_n) \mid x_i \in B \text{ for } 1 \le i \le n\}$ is the set of all possible n-tuples of 0s and 1s. The variable x is called a **Boolean variable** if it assumes values only from B, that is, if its only possible values are 0 and 1. A function from B^n to B is called a **Boolean function of degree** n.

EXAMPLE 4 The function $F(x, y) = x\overline{y}$ from the set of ordered pairs of Boolean variables to the set $\{0, 1\}$ is a Boolean function of degree 2 with F(1, 1) = 0, F(1, 0) = 1, F(0, 1) = 0, and F(0, 0) = 0. We display these values of F in Table 1.





©Alfred Eisenstaedt/The LIFE Picture Collection/ Getty Images

CLAUDE ELWOOD SHANNON (1916–2001) Claude Shannon was born in Petoskey, Michigan, and grew up in Gaylord, Michigan. His father was a businessman and a probate judge, and his mother was a language teacher and a high school principal. Shannon attended the University of Michigan, graduating in 1936. He continued his studies at M.I.T., where he took the job of maintaining the differential analyzer, a mechanical computing device consisting of shafts and gears built by his professor, Vannevar Bush. Shannon's master's thesis, written in 1936, studied the logical aspects of the differential analyzer. This master's thesis presents the first application of Boolean algebra to the design of switching circuits; it is perhaps the most famous master's thesis of the twentieth century. He received his Ph.D. from M.I.T. in 1940. Shannon joined Bell Laboratories in 1940, where he worked on transmitting data efficiently. He was one of the first people to use bits to represent information. At Bell Laboratories he worked on determining the amount of traffic that telephone lines can carry. Shannon made many fundamental contributions to information theory. In the early 1950s he was one of the founders of the study of artificial intelligence. He joined the M.I.T. faculty in 1956, where he continued his study of information theory.

Shannon had an unconventional side. He is credited with inventing the rocket-powered Frisbee. He is also famous for riding a unicycle down the hallways of Bell Laboratories while juggling four balls. Shannon retired when he was 50 years old, publishing papers sporadically over the following 10 years. In his later years he concentrated on some pet projects, such as building a motorized pogo stick. One interesting quote from Shannon, published in *Omni Magazine* in 1987, is "I visualize a time when we will be to robots what dogs are to humans. And I am rooting for the machines."

TABLE 1					
х	у	F(x, y)			
1	1	0			
1	0	1			
0	1	0			
0	0	0			

Boolean functions can be represented using expressions made up from variables and Boolean operations. The **Boolean expressions** in the variables x_1, x_2, \dots, x_n are defined recursively as

0, 1, x_1 , x_2 , ..., x_n are Boolean expressions;

if E_1 and E_2 are Boolean expressions, then \overline{E}_1 , (E_1E_2) , and (E_1+E_2) are Boolean expressions.

Each Boolean expression represents a Boolean function. The values of this function are obtained by substituting 0 and 1 for the variables in the expression. In Section 12.2 we will show that every Boolean function can be represented by a Boolean expression.

EXAMPLE 5 Find the values of the Boolean function represented by $F(x, y, z) = xy + \overline{z}$.

Solution: The values of this function are displayed in Table 2.

TABLE 2								
x	у	z	xy	\bar{z}	$F(x, y, z) = xy + \overline{z}$			
1	1	1	1	0	1			
1	1	0	1	1	1			
1	0	1	0	0	0			
1	0	0	0	1	1			
0	1	1	0	0	0			
0	1	0	0	1	1			
0	0	1	0	0	0			
0	0	0	0	1	1			

Note that we can represent a Boolean function graphically by distinguishing the vertices of the n-cube that correspond to the n-tuples of bits where the function has value 1.

EXAMPLE 6

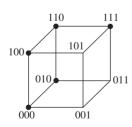


FIGURE 1

The function $F(x, y, z) = xy + \overline{z}$ from B^3 to B from Example 5 can be represented by distinguishing the vertices that correspond to the five 3-tuples (1, 1, 1), (1, 1, 0), (1, 0, 0), (0, 1, 0), and (0, 0, 0), where F(x, y, z) = 1, as shown in Figure 1. These vertices are displayed using solid black circles.

Boolean functions F and G of n variables are equal if and only if $F(b_1, b_2, ..., b_n) =$ $G(b_1, b_2, ..., b_n)$ whenever $b_1, b_2, ..., b_n$ belong to B. Two different Boolean expressions that represent the same function are called **equivalent**. For instance, the Boolean expressions xy, xy + 0, and $xy \cdot 1$ are equivalent. The **complement** of the Boolean function F is the function F, where $F(x_1, \ldots, x_n) = F(x_1, \ldots, x_n)$. Let F and G be Boolean functions of degree n. The **Boolean** sum F + G and the Boolean product FG are defined by

$$(F+G)(x_1, \dots, x_n) = F(x_1, \dots, x_n) + G(x_1, \dots, x_n),$$

 $(FG)(x_1, \dots, x_n) = F(x_1, \dots, x_n)G(x_1, \dots, x_n).$

A Boolean function of degree two is a function from a set with four elements, namely, pairs of elements from $B = \{0, 1\}$, to B, a set with two elements. Hence, there are 16 different Boolean functions of degree two. In Table 3 we display the values of the 16 different Boolean functions of degree two, labeled F_1, F_2, \ldots, F_{16} .

TΔ	TABLE 3 The 16 Boolean Functions of Degree Two.																
x	у	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F ₁₁	F_{12}	F ₁₃	F ₁₄	F ₁₅	F_{16}
1	1	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	0
1	0	1	1	1	1	0	0	0	0	1	1	1	1	0	0	0	0
0	1	1	1	0	0	1	1	0	0	1	1	0	0	1	1	0	0
0	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0

EXAMPLE 7 How many different Boolean functions of degree *n* are there?

Solution: From the product rule for counting, it follows that there are 2^n different n-tuples of 0s and 1s. Because a Boolean function is an assignment of 0 or 1 to each of these 2^n different n-tuples, the product rule shows that there are 2²ⁿ different Boolean functions of degree n.

Table 4 displays the number of different Boolean functions of degrees one through six. The number of such functions grows extremely rapidly.

TABLE 4 The Number of Boolean Functions of Degree <i>n</i> .					
Degree	Number				
1	4				
2	16				
3	256				
4	65,536				
5	4,294,967,296				
6	18,446,744,073,709,551,616				

12.1.3 **Identities of Boolean Algebra**

There are many identities in Boolean algebra. The most important of these are displayed in Table 5. These identities are particularly useful in simplifying the design of circuits. Each of the identities in Table 5 can be proved using a table. We will prove one of the distributive laws in this way in Example 8. The proofs of the remaining properties are left as exercises for the reader.

EXAMPLE 8 Show that the distributive law x(y + z) = xy + xz is valid.

Solution: The verification of this identity is shown in Table 6. The identity holds because the last two columns of the table agree.

The reader should compare the Boolean identities in Table 5 to the logical equivalences in Table 6 of Section 1.3 and the set identities in Table 1 in Section 2.2. All are special cases of the same set of identities in a more abstract structure. Each collection of identities can be obtained by making the appropriate translations. For example, we can transform each of the identities in

TABLE 5 Boolean Identities.				
Identity	Name			
$\overline{\overline{x}} = x$	Law of the double complement			
$x + x = x$ $x \cdot x = x$	Idempotent laws			
$x + 0 = x$ $x \cdot 1 = x$	Identity laws			
$x + 1 = 1$ $x \cdot 0 = 0$	Domination laws			
x + y = y + x $xy = yx$	Commutative laws			
x + (y + z) = (x + y) + z $x(yz) = (xy)z$	Associative laws			
x + yz = (x + y)(x + z) $x(y + z) = xy + xz$	Distributive laws			
$\overline{(xy)} = \overline{x} + \overline{y}$ $\overline{(x+y)} = \overline{x}\overline{y}$	De Morgan's laws			
x + xy = x $x(x + y) = x$	Absorption laws			
$x + \overline{x} = 1$	Unit property			
$x\overline{x} = 0$	Zero property			

Compare these Boolean identities with the logical equivalences in Section 1.3 and the set identities in Section 2.2.

> Table 5 into a logical equivalence by changing each Boolean variable into a propositional variable, each 0 into a F, each 1 into a T, each Boolean sum into a disjunction, each Boolean product into a conjunction, and each complementation into a negation, as we illustrate in Example 9.

EXAMPLE 9 Translate the distributive law x + yz = (x + y)(x + z) in Table 5 into a logical equivalence.

Solution: To translate a Boolean identity into a logical equivalence, we change each Boolean variable into a propositional variable. Here we will change the Boolean variables x, y, and z into the propositional variables p, q, and r. Next, we change each Boolean sum into a disjunction and

TABL	TABLE 6 Verifying One of the Distributive Laws.								
x	у	z	y + z	xy	xz	x(y+z)	xy + xz		
1	1	1	1	1	1	1	1		
1	1	0	1	1	0	1	1		
1	0	1	1	0	1	1	1		
1	0	0	0	0	0	0	0		
0	1	1	1	0	0	0	0		
0	1	0	1	0	0	0	0		
0	0	1	1	0	0	0	0		
0	0	0	0	0	0	0	0		

each Boolean product into a conjunction. (Note that 0 and 1 do not appear in this identity and complementation also does not appear.) This transforms the Boolean identity into the logical equivalence

$$p \lor (q \land r) \equiv (p \lor q) \land (p \lor r).$$

This logical equivalence is one of the distributive laws for propositional logic in Table 6 in Section 1.3.

Identities in Boolean algebra can be used to prove further identities. We demonstrate this in Example 10.

EXAMPLE 10

Prove the **absorption law** x(x + y) = x using the other identities of Boolean algebra shown in Table 5. (This is called an absorption law because absorbing x + y into x leaves x unchanged.)



Solution: We display steps used to derive this identity and the law used in each step:

$$x(x + y) = (x + 0)(x + y)$$
 Identity law for the Boolean sum
$$= x + 0 \cdot y$$
 Distributive law of the Boolean sum over the Boolean product
$$= x + y \cdot 0$$
 Commutative law for the Boolean product
$$= x + 0$$
 Domination law for the Boolean product
$$= x$$
 Identity law for the Boolean sum.

12.1.4 Duality

The identities in Table 5 come in pairs (except for the law of the double complement and the unit and zero properties). To explain the relationship between the two identities in each pair we use the concept of a dual. The **dual** of a Boolean expression is obtained by interchanging Boolean sums and Boolean products and interchanging 0s and 1s.

EXAMPLE 11 Find the duals of x(y + 0) and $\bar{x} \cdot 1 + (\bar{y} + z)$.

Solution: Interchanging \cdot signs and + signs and interchanging 0s and 1s in these expressions produces their duals. The duals are $x + (y \cdot 1)$ and $(\bar{x} + 0)(\bar{y}z)$, respectively.

The dual of a Boolean function F represented by a Boolean expression is the function represented by the dual of this expression. This dual function, denoted by F^d , does not depend on the particular Boolean expression used to represent F. An identity between functions represented by Boolean expressions remains valid when the duals of both sides of the identity are taken. (See Exercise 30 for the reason why this is true.) This result, called the **duality principle**, is useful for obtaining new identities.

EXAMPLE 12 Construct an identity from the absorption law x(x + y) = x by taking duals.

Solution: Taking the duals of both sides of this identity produces the identity x + xy = x, which is also called an absorption law and is shown in Table 5.

The Abstract Definition of a Boolean Algebra

In this section we have focused on Boolean functions and expressions. However, the results we have established can be translated into results about propositions or results about sets. Because of this, it is useful to define Boolean algebras abstractly. Once it is shown that a particular structure is a Boolean algebra, then all results established about Boolean algebras in general apply to this particular structure.

Boolean algebras can be defined in several ways. The most common way is to specify the properties that operations must satisfy, as is done in Definition 1.

Definition 1

A Boolean algebra is a set B with two binary operations \vee and \wedge , elements 0 and 1, and a unary operation $\overline{}$ such that these properties hold for all x, y, and z in B:

$$x \lor 0 = x \\ x \land 1 = x$$
 Identity laws
$$x \lor \overline{x} = 1 \\ x \land \overline{x} = 0$$
 Complement laws
$$(x \lor y) \lor z = x \lor (y \lor z) \\ (x \land y) \land z = x \land (y \land z)$$
 Associative laws
$$x \lor y = y \lor x \\ x \land y = y \land x$$
 Commutative laws
$$x \lor (y \land z) = (x \lor y) \land (x \lor z) \\ x \land (y \lor z) = (x \land y) \lor (x \land z)$$
 Distributive laws

Using the laws given in Definition 1, it is possible to prove many other laws that hold for every Boolean algebra, such as idempotent and domination laws. (See Exercises 35–42.)

From our previous discussion, $B = \{0, 1\}$ with the OR and AND operations and the complement operator, satisfies all these properties. The set of propositions in n variables, with the \vee and \wedge operators, **F** and **T**, and the negation operator, also satisfies all the properties of a Boolean algebra, as can be seen from Table 6 in Section 1.3. Similarly, the set of subsets of a universal set U with the union and intersection operations, the empty set and the universal set, and the set complementation operator, is a Boolean algebra as can be seen by consulting Table 1 in Section 2.2. So, to establish results about each of Boolean expressions, propositions, and sets, we need only prove results about abstract Boolean algebras.

Boolean algebras may also be defined using the notion of a lattice, discussed in Chapter 9. Recall that a lattice L is a partially ordered set in which every pair of elements x, y has a least upper bound, denoted by lub(x, y) and a greatest lower bound denoted by glb(x, y). Given two elements x and y of L, we can define two operations \vee and \wedge on pairs of elements of L by $x \lor y = \text{lub}(x, y) \text{ and } x \land y = \text{glb}(x, y).$

For a lattice L to be a Boolean algebra as specified in Definition 1, it must have two properties. First, it must be **complemented**. For a lattice to be complemented it must have a least element 0 and a greatest element 1 and for every element x of the lattice there must exist an element \bar{x} such that $x \vee \bar{x} = 1$ and $x \wedge \bar{x} = 0$. Second, it must be **distributive**. This means that for every x, y, and z in L, $x \lor (y \land z) = (x \lor y) \land (x \lor z)$ and $x \land (y \lor z) = (x \land y) \lor (x \land z)$. Showing that a complemented, distributive lattice is a Boolean algebra has been left as Supplementary Exercise 39 in Chapter 9.

Exercises

- 1. Find the values of these expressions.
 - a) $1 \cdot \overline{0}$
- **b**) $1 + \overline{1}$
- c) $\overline{0} \cdot 0$
- **d**) $\overline{(1+0)}$
- **2.** Find the values, if any, of the Boolean variable *x* that satisfy these equations.
 - **a**) $x \cdot 1 = 0$
- **b**) x + x = 0
- **c**) $x \cdot 1 = x$
- **d**) $x \cdot \overline{x} = 1$
- **3. a)** Show that $(1 \cdot 1) + (\overline{0 \cdot 1} + 0) = 1$.
 - b) Translate the equation in part (a) into a propositional equivalence by changing each 0 into an F, each 1 into a T, each Boolean sum into a disjunction, each Boolean product into a conjunction, each complementation into a negation, and the equals sign into a propositional equivalence sign.
- **4. a)** Show that $(\overline{1} \cdot \overline{0}) + (1 \cdot \overline{0}) = 1$.
 - b) Translate the equation in part (a) into a propositional equivalence by changing each 0 into an **F**, each 1 into a **T**, each Boolean sum into a disjunction, each Boolean product into a conjunction, each complementation into a negation, and the equals sign into a propositional equivalence sign.
- **5.** Use a table to express the values of each of these Boolean functions.
 - **a**) $F(x, y, z) = \overline{x}y$
 - **b**) F(x, y, z) = x + yz
 - c) $F(x, y, z) = x\overline{y} + \overline{(xyz)}$
 - **d**) $F(x, y, z) = x(yz + \overline{y}\overline{z})$
- **6.** Use a table to express the values of each of these Boolean functions.
 - a) $F(x, y, z) = \overline{z}$
 - **b)** $F(x, y, z) = \overline{x}y + \overline{y}z$
 - c) $F(x, y, z) = x\overline{y}z + \overline{(xyz)}$
 - **d**) $F(x, y, z) = \overline{y}(xz + \overline{x}\overline{z})$
- 7. Use a 3-cube Q_3 to represent each of the Boolean functions in Exercise 5 by displaying a black circle at each vertex that corresponds to a 3-tuple where this function has the value 1.
- **8.** Use a 3-cube Q_3 to represent each of the Boolean functions in Exercise 6 by displaying a black circle at each vertex that corresponds to a 3-tuple where this function has the value 1.
- **9.** What values of the Boolean variables x and y satisfy xy = x + y?
- **10.** How many different Boolean functions are there of degree 7?
- 11. Prove the absorption law x + xy = x using the other laws in Table 5.
- **12.** Show that F(x, y, z) = xy + xz + yz has the value 1 if and only if at least two of the variables x, y, and z have the value 1.
 - 13. Show that $x\overline{y} + y\overline{z} + \overline{x}z = \overline{x}y + \overline{y}z + x\overline{z}$.

Exercises 14–23 deal with the Boolean algebra {0, 1} with addition, multiplication, and complement defined at the beginning of this section. In each case, use a table as in Example 8.

- **14.** Verify the law of the double complement.
- 15. Verify the idempotent laws.
- **16.** Verify the identity laws.
- 17. Verify the domination laws.
- 18. Verify the commutative laws.
- 19. Verify the associative laws.
- **20.** Verify the first distributive law in Table 5.
- 21. Verify De Morgan's laws.
- 22. Verify the unit property.
- 23. Verify the zero property.

The Boolean operator \oplus , called the *XOR* operator, is defined by $1 \oplus 1 = 0$, $1 \oplus 0 = 1$, $0 \oplus 1 = 1$, and $0 \oplus 0 = 0$.

- **24.** Simplify these expressions.
 - a) $x \oplus 0$
- **b**) $x \oplus 1$
- c) $x \oplus x$
- **d**) $x \oplus \overline{x}$
- 25. Show that these identities hold.
 - a) $x \oplus y = (x + y)(\overline{xy})$
 - **b**) $x \oplus y = (x\overline{y}) + (\overline{x}y)$
- **26.** Show that $x \oplus y = y \oplus x$.
- **27.** Prove or disprove these equalities.
 - a) $x \oplus (y \oplus z) = (x \oplus y) \oplus z$
 - **b)** $x + (y \oplus z) = (x + y) \oplus (x + z)$
 - c) $x \oplus (y + z) = (x \oplus y) + (x \oplus z)$
- **28.** Find the duals of these Boolean expressions.
 - a) x + y
- **b**) $\bar{x}\bar{y}$
- c) $xyz + \overline{x}\overline{y}\overline{z}$
- **d**) $x\overline{z} + x \cdot 0 + \overline{x} \cdot 1$
- *29. Suppose that F is a Boolean function represented by a Boolean expression in the variables x_1, \ldots, x_n . Show that $F^d(x_1, \ldots, x_n) = \overline{F(\overline{x}_1, \ldots, \overline{x}_n)}$.
- *30. Show that if F and G are Boolean functions represented by Boolean expressions in n variables and F = G, then $F^d = G^d$, where F^d and G^d are the Boolean functions represented by the duals of the Boolean expressions representing F and G, respectively. [Hint: Use the result of Exercise 29.]
- *31. How many different Boolean functions F(x, y, z) are there such that $F(\overline{x}, \overline{y}, \overline{z}) = F(x, y, z)$ for all values of the Boolean variables x, y, and z?
- *32. How many different Boolean functions F(x, y, z) are there such that $F(\bar{x}, y, z) = F(x, \bar{y}, z) = F(x, y, \bar{z})$ for all values of the Boolean variables x, y, y and z?
- **33.** Show that you obtain De Morgan's laws for propositions (in Table 6 in Section 1.3) when you transform De Morgan's laws for Boolean algebra in Table 6 into logical equivalences.
- **34.** Show that you obtain the absorption laws for propositions (in Table 6 in Section 1.3) when you transform the absorption laws for Boolean algebra in Table 6 into logical equivalences.

In Exercises 35–42, use the laws in Definition 1 to show that the stated properties hold in every Boolean algebra.

- 35. Show that in a Boolean algebra, the idempotent laws $x \lor x = x$ and $x \land x = x$ hold for every element x.
- **36.** Show that in a Boolean algebra, every element x has a unique complement \bar{x} such that $x \vee \bar{x} = 1$ and $x \wedge \bar{x} = 0$.
- 37. Show that in a Boolean algebra, the complement of the element 0 is the element 1 and vice versa.
- 38. Prove that in a Boolean algebra, the law of the double **complement** holds; that is, $\bar{x} = x$ for every element x.
- 39. Show that De Morgan's laws hold in a Boolean algebra.

- That is, show that for all x and y, $\overline{(x \lor y)} = \overline{x} \land \overline{y}$ and $\overline{(x \wedge y)} = \overline{x} \vee \overline{y}.$
- **40.** Show that in a Boolean algebra, the **modular properties** hold. That is, show that $x \land (y \lor (x \land z)) = (x \land y) \lor (x \land z)$ z) and $x \lor (y \land (x \lor z)) = (x \lor y) \land (x \lor z)$.
- **41.** Show that in a Boolean algebra, if $x \lor y = 0$, then x = 0and y = 0, and that if $x \wedge y = 1$, then x = 1 and y = 1.
- 42. Show that in a Boolean algebra, the dual of an identity, obtained by interchanging the \vee and \wedge operators and interchanging the elements 0 and 1, is also a valid identity.
- 43. Show that a complemented, distributive lattice is a Boolean algebra.

Representing Boolean Functions

Two important problems of Boolean algebra will be studied in this section. The first problem is: Given the values of a Boolean function, how can a Boolean expression that represents this function be found? This problem will be solved by showing that any Boolean function can be represented by a Boolean sum of Boolean products of the variables and their complements. The solution of this problem shows that every Boolean function can be represented using the three Boolean operators , +, and -. The second problem is: Is there a smaller set of operators that can be used to represent all Boolean functions? We will answer this question by showing that all Boolean functions can be represented using only one operator. Both of these problems have practical importance in circuit design.

Sum-of-Products Expansions

We will use examples to illustrate one important way to find a Boolean expression that represents a Boolean function.

EXAMPLE 1

Find Boolean expressions that represent the functions F(x, y, z) and G(x, y, z), which are given in Table 1.

TA	TABLE 1					
x	у	z	F	G		
1	1	1	0	0		
1	1	0	0	1		
1	0	1	1	0		
1	0	0	0	0		
0	1	1	0	0		
0	1	0	0	1		
0	0	1	0	0		
0	0	0	0	0		

Solution: An expression that has the value 1 when x = z = 1 and y = 0, and the value 0 otherwise, is needed to represent F. Such an expression can be formed by taking the Boolean product of x, \overline{y} , and z. This product, $x\overline{y}z$, has the value 1 if and only if $x = \overline{y} = z = 1$, which holds if and only if x = z = 1 and y = 0.

To represent G, we need an expression that equals 1 when x = y = 1 and z = 0, or x = z = 0and y = 1. We can form an expression with these values by taking the Boolean sum of two different Boolean products. The Boolean product $xy\overline{z}$ has the value 1 if and only if x = y = 1and z = 0. Similarly, the product $\overline{x}y\overline{z}$ has the value 1 if and only if x = z = 0 and y = 1. The Boolean sum of these two products, $xy\overline{z} + \overline{x}y\overline{z}$, represents G, because it has the value 1 if and only if x = y = 1 and z = 0, or x = z = 0 and y = 1.

Example 1 illustrates a procedure for constructing a Boolean expression representing a function with given values. Each combination of values of the variables for which the function has the value 1 leads to a Boolean product of the variables or their complements.

Definition 1

A *literal* is a Boolean variable or its complement. A *minterm* of the Boolean variables x_1, x_2, \ldots, x_n is a Boolean product $y_1 y_2 \cdots y_n$, where $y_i = x_i$ or $y_i = \overline{x}_i$. Hence, a minterm is a product of n literals, with one literal for each variable.

A minterm has the value 1 for one and only one combination of values of its variables. More precisely, the minterm $y_1y_2...y_n$ is 1 if and only if each y_i is 1, and this occurs if and only if $x_i = 1$ when $y_i = x_i$ and $x_i = 0$ when $y_i = \overline{x_i}$.

EXAMPLE 2 Find a minterm that equals 1 if $x_1 = x_3 = 0$ and $x_2 = x_4 = x_5 = 1$, and equals 0 otherwise.

Solution: The minterm $\bar{x}_1 x_2 \bar{x}_3 x_4 x_5$ has the correct set of values.

By taking Boolean sums of distinct minterms we can build up a Boolean expression with a specified set of values. In particular, a Boolean sum of minterms has the value 1 when exactly one of the minterms in the sum has the value 1. It has the value 0 for all other combinations of values of the variables. Consequently, given a Boolean function, a Boolean sum of minterms can be formed that has the value 1 when this Boolean function has the value 1, and has the value 0 when the function has the value 0. The minterms in this Boolean sum correspond to those combinations of values for which the function has the value 1. The sum of minterms that represents the function is called the **sum-of-products expansion** or the **disjunctive normal form** of the Boolean function.

Links

(See Exercise 46 in Section 1.3 for the development of disjunctive normal form in propositional calculus.)

EXAMPLE 3 Find the sum-of-products expansion for the function $F(x, y, z) = (x + y)\overline{z}$.

Extra Examples *Solution:* We will find the sum-of-products expansion of F(x, y, z) in two ways. First, we will use Boolean identities to expand the product and simplify. We find that

$$F(x, y, z) = (x + y)\overline{z}$$

$$= x\overline{z} + y\overline{z}$$
Distributive law
$$= x1\overline{z} + 1y\overline{z}$$
Identity law
$$= x(y + \overline{y})\overline{z} + (x + \overline{x})y\overline{z}$$
Unit property
$$= xy\overline{z} + x\overline{y}\overline{z} + xy\overline{z} + \overline{x}y\overline{z}$$
Distributive law
$$= xy\overline{z} + x\overline{y}\overline{z} + x\overline{y}\overline{z}.$$
Idempotent law

Second, we can construct the sum-of-products expansion by determining the values of F for all possible values of the variables x, y, and z. These values are found in Table 2. The sum-of-products expansion of F is the Boolean sum of three minterms corresponding to the three rows of this table that give the value 1 for the function. This gives

$$F(x, y, z) = xy\overline{z} + x\overline{y}\overline{z} + \overline{x}y\overline{z}.$$

It is also possible to find a Boolean expression that represents a Boolean function by taking a Boolean product of Boolean sums. The resulting expansion is called the **conjunctive normal form** or **product-of-sums expansion** of the function. These expansions can be found from sum-of-products expansions by taking duals. How to find such expansions directly is described in Exercise 10.

TABLE 2							
х	у	z	x + y	\bar{z}	$(x+y)\overline{z}$		
1	1	1	1	0	0		
1	1	0	1	1	1		
1	0	1	1	0	0		
1	0	0	1	1	1		
0	1	1	1	0	0		
0	1	0	1	1	1		
0	0	1	0	0	0		
0	0	0	0	1	0		

12.2.2 Functional Completeness

Every Boolean function can be expressed as a Boolean sum of minterms. Each minterm is the Boolean product of Boolean variables or their complements. This shows that every Boolean function can be represented using the Boolean operators , +, and -. Because every Boolean function can be represented using these operators we say that the set $\{\cdot, +, -\}$ is **functionally** complete. Can we find a smaller set of functionally complete operators? We can do so if one of the three operators of this set can be expressed in terms of the other two. This can be done using one of De Morgan's laws. We can eliminate all Boolean sums using the identity

$$x + y = \overline{\overline{x}}\overline{y}$$

which is obtained by taking complements of both sides in the second De Morgan law, given in Table 5 in Section 12.1, and then applying the double complementation law. This means that the set $\{\cdot, -\}$ is functionally complete. Similarly, we could eliminate all Boolean products using the identity

$$xy = \overline{\overline{x} + \overline{y}},$$

which is obtained by taking complements of both sides in the first De Morgan law, given in Table 5 in Section 12.1, and then applying the double complementation law. Consequently $\{+,-\}$ is functionally complete. Note that the set $\{+,\cdot\}$ is not functionally complete, because it is impossible to express the Boolean function $F(x) = \overline{x}$ using these operators (see Exercise 19).



We have found sets containing two operators that are functionally complete. Can we find a smaller set of functionally complete operators, namely, a set containing just one operator? Such sets exist. Define two operators, the \mid or *NAND* operator, defined by $1 \mid 1 = 0$ and $1 \mid 0 = 0 \mid 1 = 0 \mid 0 = 1$; and the \downarrow or **NOR** operator, defined by $1 \downarrow 1 = 1 \downarrow 0 = 0 \downarrow 1 = 0$ and $0 \downarrow 0 = 1$. Both of the sets { | } and { \downarrow } are functionally complete. To see that { | } is functionally complete, because $\{\cdot, -\}$ is functionally complete, all that we have to do is show that both of the operators \cdot and $\overline{\ }$ can be expressed using just the | operator. This can be done as

$$\overline{x} = x \mid x$$
,
 $xy = (x \mid y) \mid (x \mid y)$.

The reader should verify these identities (see Exercise 14). We leave the demonstration that $\{\downarrow\}$ is functionally complete for the reader (see Exercises 15 and 16).

858

- 1. Find a Boolean product of the Boolean variables x, y, and z, or their complements, that has the value 1 if and only if
 - **a**) x = y = 0, z = 1.
- **b**) x = 0, y = 1, z = 0.
- **c**) x = 0, y = z = 1.
- **d**) x = y = z = 0.
- 2. Find the sum-of-products expansions of these Boolean functions.
 - a) $F(x, y) = \overline{x} + y$
- c) F(x, y) = 1
- **b)** $F(x, y) = x \bar{y}$ **d)** $F(x, y) = \bar{y}$
- 3. Find the sum-of-products expansions of these Boolean functions.
 - **a)** F(x, y, z) = x + y + z
 - **b**) F(x, y, z) = (x + z)y
 - **c**) F(x, y, z) = x
 - **d**) $F(x, y, z) = x \overline{y}$
- **4.** Find the sum-of-products expansions of the Boolean function F(x, y, z) that equals 1 if and only if
 - **a**) x = 0.
- **b**) xy = 0.
- **c**) x + y = 0.
- **d**) xyz = 0.
- 5. Find the sum-of-products expansion of the Boolean function F(w, x, y, z) that has the value 1 if and only if an odd number of w, x, y, and z have the value 1.
- **6.** Find the sum-of-products expansion of the Boolean function $F(x_1, x_2, x_3, x_4, x_5)$ that has the value 1 if and only if three or more of the variables x_1, x_2, x_3, x_4 , and x_5 have the value 1.

Another way to find a Boolean expression that represents a Boolean function is to form a Boolean product of Boolean sums of literals. Exercises 7–11 are concerned with representations of this kind.

- 7. Find a Boolean sum containing either x or \bar{x} , either y or \overline{y} , and either z or \overline{z} that has the value 0 if and only if
 - **a)** x = y = 1, z = 0.
- **b**) x = y = z = 0.
- c) x = z = 0, y = 1.
- 8. Find a Boolean product of Boolean sums of literals that has the value 0 if and only if x = y = 1 and z = 0, x = z =0 and y = 1, or x = y = z = 0. [Hint: Take the Boolean product of the Boolean sums found in parts (a), (b), and (c) in Exercise 7.]

Logic Gates

- **9.** Show that the Boolean sum $y_1 + y_2 + \cdots + y_n$, where $y_i =$ x_i or $y_i = \overline{x}_i$, has the value 0 for exactly one combination of the values of the variables, namely, when $x_i = 0$ if $y_i = x_i$ and $x_i = 1$ if $y_i = \overline{x}_i$. This Boolean sum is called a maxterm.
- 10. Show that a Boolean function can be represented as a Boolean product of maxterms. This representation is called the product-of-sums expansion or conjunctive normal form of the function. [Hint: Include one maxterm in this product for each combination of the variables where the function has the value 0.]
- 11. Find the product-of-sums expansion of each of the Boolean functions in Exercise 3.
- 12. Express each of these Boolean functions using the operators \cdot and $^-$.
 - a) x + y + z
- **b**) $x + \overline{y}(\overline{x} + z)$

- **d**) $\overline{x}(x+\overline{y}+\overline{z})$
- 13. Express each of the Boolean functions in Exercise 12 using the operators + and $\bar{}$.
- 14. Show that
 - a) $\bar{x} = x \mid x$.
- **b)** $xy = (x \mid y) \mid (x \mid y)$.
- **c**) $x + y = (x \mid x) \mid (y \mid y)$.
- 15. Show that
 - a) $\bar{x} = x \downarrow x$.
 - **b)** $xy = (x \downarrow x) \downarrow (y \downarrow y).$
 - c) $x + y = (x \downarrow y) \downarrow (x \downarrow y)$.
- **16.** Show that $\{\downarrow\}$ is functionally complete using Exer-
- 17. Express each of the Boolean functions in Exercise 3 using the operator |.
- 18. Express each of the Boolean functions in Exercise 3 using the operator \downarrow .
- **19.** Show that the set of operators $\{+,\cdot\}$ is not functionally complete.
- **20.** Are these sets of operators functionally complete?
 - a) $\{+, \oplus\}$
- **b**) {¯, ⊕}
- c) $\{\cdot, \oplus\}$

Links

Introduction 12.3.1

Boolean algebra is used to model the circuitry of electronic devices. Each input and each output of such a device can be thought of as a member of the set {0, 1}. A computer, or other electronic device, is made up of a number of circuits. Each circuit can be designed using the rules of Boolean algebra that were studied in Sections 12.1 and 12.2. The basic elements of circuits are called gates, and were introduced in Section 1.2. Each type of gate implements a Boolean operation. In this section we define several types of gates. Using these gates, we will apply the

FIGURE 1 Basic types of gates.

rules of Boolean algebra to design circuits that perform a variety of tasks. The circuits that we will study in this chapter give output that depends only on the input, and not on the current state of the circuit. In other words, these circuits have no memory capabilities. Such circuits are called **combinational circuits** or **gating networks**.

We will construct combinational circuits using three types of elements. The first is an **inverter**, which accepts the value of one Boolean variable as input and produces the complement of this value as its output. The symbol used for an inverter is shown in Figure 1(a). The input to the inverter is shown on the left side entering the element, and the output is shown on the right side leaving the element.

The next type of element we will use is the **OR gate**. The inputs to this gate are the values of two or more Boolean variables. The output is the Boolean sum of their values. The symbol used for an OR gate is shown in Figure 1(b). The inputs to the OR gate are shown on the left side entering the element, and the output is shown on the right side leaving the element.

The third type of element we will use is the **AND gate**. The inputs to this gate are the values of two or more Boolean variables. The output is the Boolean product of their values. The symbol used for an AND gate is shown in Figure 1(c). The inputs to the AND gate are shown on the left side entering the element, and the output is shown on the right side leaving the element.

We will permit multiple inputs to AND and OR gates. The inputs to each of these gates are shown on the left side entering the element, and the output is shown on the right side. Examples of AND and OR gates with n inputs are shown in Figure 2.

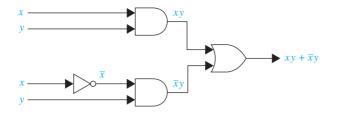


FIGURE 2 Gates with n inputs.

12.3.2 Combinations of Gates

Combinational circuits can be constructed using a combination of inverters, OR gates, and AND gates. When combinations of circuits are formed, some gates may share inputs. This is shown in one of two ways in depictions of circuits. One method is to use branchings that indicate all the gates that use a given input. The other method is to indicate this input separately for each gate. Figure 3 illustrates the two ways of showing gates with the same input values. Note also that output from a gate may be used as input by one or more other elements, as shown in Figure 3. Both drawings in Figure 3 depict the circuit that produces the output $xy + \overline{x}y$.

EXAMPLE 1 Construct circuits that produce the following outputs: (a) $(x + y)\overline{x}$, (b) $\overline{x}(y + \overline{z})$, and (c) $(x + y + z)(\overline{x}\overline{y}\overline{z})$.



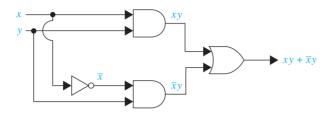


FIGURE 3 Two ways to draw the same circuit.

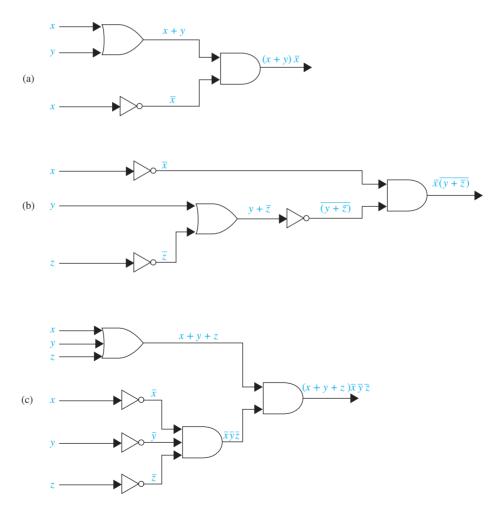


FIGURE 4 Circuits that produce the outputs specified in Example 1.

12.3.3 Examples of Circuits

We will give some examples of circuits that perform some useful functions.

EXAMPLE 2

A committee of three individuals decides issues for an organization. Each individual votes either yes or no for each proposal that arises. A proposal is passed if it receives at least two yes votes. Design a circuit that determines whether a proposal passes.



Solution: Let x = 1 if the first individual votes yes, and x = 0 if this individual votes no; let y = 1 if the second individual votes ves, and y = 0 if this individual votes no; let z = 1 if the third individual votes yes, and z = 0 if this individual votes no. Then a circuit must be designed that produces the output 1 from the inputs x, y, and z when two or more of x, y, and z are 1. One representation of the Boolean function that has these output values is xy + xz + yz (see Exercise 12 in Section 12.1). The circuit that implements this function is shown in Figure 5.

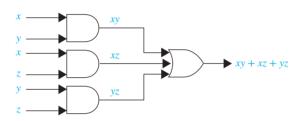


FIGURE 5 A circuit for majority voting.

EXAMPLE 3

Sometimes light fixtures are controlled by more than one switch. Circuits need to be designed so that flipping any one of the switches for the fixture turns the light on when it is off and turns the light off when it is on. Design circuits that accomplish this when there are two switches and when there are three switches.

TABLE 1						
x	x y $F(x,y)$					
1	1	1				
1	0	0				
0	1	0				
0	0	1				

Solution: We will begin by designing the circuit that controls the light fixture when two different switches are used. Let x = 1 when the first switch is closed and x = 0 when it is open, and let y = 1 when the second switch is closed and y = 0 when it is open. Let F(x, y) = 1 when the light is on and F(x, y) = 0 when it is off. We can arbitrarily decide that the light will be on when both switches are closed, so that F(1,1) = 1. This determines all the other values of F. When one of the two switches is opened, the light goes off, so F(1,0) = F(0,1) = 0. When the other switch is also opened, the light goes on, so F(0,0) = 1. Table 1 displays these values. Note that $F(x, y) = xy + \overline{x}\overline{y}$. This function is implemented by the circuit shown in Figure 6.

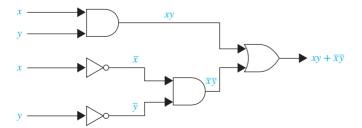


FIGURE 6 A circuit for a light controlled by two switches.

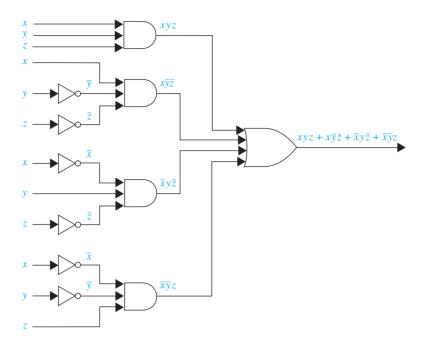


FIGURE 7 A circuit for a fixture controlled by three switches.

T	TABLE 2						
x	у	y z F(x, y)					
1	1	1	1				
1	1	0	0				
1	0	1	0				
1	0	0	1				
0	1	1	0				
0	1	0	1				
0	0	1	1				
0	0	0	0				

We will now design a circuit for three switches. Let x, y, and z be the Boolean variables that indicate whether each of the three switches is closed. We let x = 1 when the first switch is closed, and x = 0 when it is open; y = 1 when the second switch is closed, and y = 0 when it is open; and z = 1 when the third switch is closed, and z = 0 when it is open. Let F(x, y, z) = 1 when the light is on and F(x, y, z) = 0 when the light is off. We can arbitrarily specify that the light be on when all three switches are closed, so that F(1, 1, 1) = 1. This determines all other values of F(1, 1, 1) = 1. When one switch is opened, the light goes off, so F(1, 1, 0) = F(1, 0, 1) = F(0, 1, 1) = 0. When a second switch is opened, the light goes on, so F(1, 0, 0) = F(0, 1, 0) = F(0, 0, 1) = 1. Finally, when the third switch is opened, the light goes off again, so F(0, 0, 0) = 0. Table 2 shows the values of this function.

The function F can be represented by its sum-of-products expansion as $F(x, y, z) = xyz + x\overline{y}\overline{z} + \overline{x}y\overline{z} + \overline{x}\overline{y}z$. The circuit shown in Figure 7 implements this function.

Links

12.3.4 Adders

TABLE 3 Input and Output for the Half Adder.

Inp	out	Output			
x	у	S	с		
1	1	0	1		
1	0	1	0		
0	1	1	0		
0	0	0	0		

We will illustrate how logic circuits can be used to carry out addition of two positive integers from their binary expansions. We will build up the circuitry to do this addition from some component circuits. First, we will build a circuit that can be used to find x + y, where x and y are two bits. The input to our circuit will be x and y, because these each have the value 0 or the value 1. The output will consist of two bits, namely, s and c, where s is the sum bit and c is the carry bit. This circuit is called a **multiple output circuit** because it has more than one output. The circuit that we are designing is called the **half adder**, because it adds two bits, without considering a carry from a previous addition. We show the input and output for the half adder in Table 3. From Table 3 we see that c = xy and that $s = x\overline{y} + \overline{x}y = (x + y)\overline{(xy)}$. Hence, the circuit shown in Figure 8 computes the sum bit s and the carry bit s from the bits s and s.

We use the **full adder** to compute the sum bit and the carry bit when two bits and a carry are added. The inputs to the full adder are the bits x and y and the carry c_i . The outputs are the sum bit s and the new carry c_{i+1} . The inputs and outputs for the full adder are shown in Table 4.

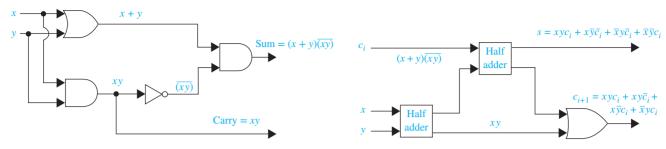


FIGURE 8 The half adder.

FIGURE 9 A full adder.

TABLE 4 Input and Output for the Full Adder.						
1	при	ıt	Output			
x	у	c_{i}	s	c_{i+1}		
1	1	1	1	1		
1	1	0	0	1		
1	0	1	0	1		
_	_	_		_		

0 1

0

0 1 0

The two outputs of the full adder, the sum bit s and the carry c_{i+1} , are given by the sum-ofproducts expansions $xyc_i + x\overline{y}\overline{c}_i + \overline{x}y\overline{c}_i + \overline{x}\overline{y}c_i$ and $xyc_i + xy\overline{c}_i + \overline{x}yc_i + \overline{x}yc_i$, respectively. However, instead of designing the full adder from scratch, we will use half adders to produce the desired output. A full adder circuit using half adders is shown in Figure 9.

Finally, in Figure 10 we show how full and half adders can be used to add the two three-bit integers $(x_2x_1x_0)_2$ and $(y_2y_1y_0)_2$ to produce the sum $(s_3s_2s_1s_0)_2$. Note that s_3 , the highest-order bit in the sum, is given by the carry c_2 .

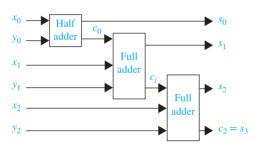


FIGURE 10 Adding two three-bit integers with full and half adders.


Exercises


0

0 0 1

0 0 0 0 0

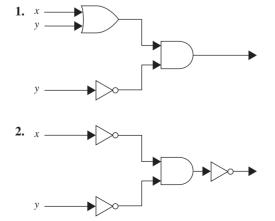
In Exercises 1–5 find the output of the given circuit.



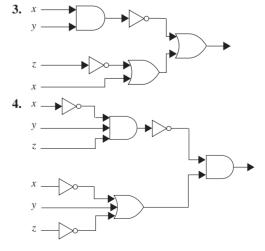

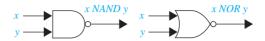- **6.** Construct circuits from inverters, AND gates, and OR gates to produce these outputs.
 - a) $\bar{x} + y$
- **b**) $\overline{(x+y)}x$
- c) $xyz + \overline{x}\overline{y}\overline{z}$
- **d**) $\overline{(\overline{x}+z)(y+\overline{z})}$
- Design a circuit that implements majority voting for five individuals.
- **8.** Design a circuit for a light fixture controlled by four switches, where flipping one of the switches turns the light on when it is off and turns it off when it is on.
- **9.** Show how the sum of two five-bit integers can be found using full and half adders.
- 10. Construct a circuit for a half subtractor using AND gates, OR gates, and inverters. A half subtractor has two bits as input and produces as output a difference bit and a borrow.
- 11. Construct a circuit for a full subtractor using AND gates, OR gates, and inverters. A **full subtractor** has two bits and a borrow as input, and produces as output a difference bit and a borrow.
- **12.** Use the circuits from Exercises 10 and 11 to find the difference of two four-bit integers, where the first integer is greater than the second integer.
- *13. Construct a circuit that compares the two-bit integers $(x_1x_0)_2$ and $(y_1y_0)_2$, returning an output of 1 when the first of these numbers is larger and an output of 0 otherwise.
- *14. Construct a circuit that computes the product of the twobit integers $(x_1x_0)_2$ and $(y_1y_0)_2$. The circuit should have four output bits for the bits in the product.

Two gates that are often used in circuits are NAND and NOR gates. When NAND or NOR gates are used to represent circuits, no other types of gates are needed. The notation for these gates is as follows:



- *15. Use NAND gates to construct circuits with these outputs.
 - a) \bar{x}

b) x + y

c) *xy*

- **d**) $x \oplus y$
- *16. Use NOR gates to construct circuits for the outputs given in Exercise 15.
- *17. Construct a half adder using NAND gates.
- *18. Construct a half adder using NOR gates.

A **multiplexer** is a switching circuit that produces as output one of a set of input bits based on the value of control bits.

19. Construct a multiplexer using AND gates, OR gates, and inverters that has as input the four bits x_0 , x_1 , x_2 , and x_3 and the two control bits c_0 and c_1 . Set up the circuit so that x_i is the output, where i is the value of the two-bit integer $(c_1c_0)_2$.

The **depth** of a combinatorial circuit can be defined by specifying that the depth of the initial input is 0 and if a gate has n different inputs at depths d_1, d_2, \ldots, d_n , respectively, then its outputs have depth equal to $\max(d_1, d_2, \ldots, d_n) + 1$; this value is also defined to be the depth of the gate. The depth of a combinatorial circuit is the maximum depth of the gates in the circuit.

- 20. Find the depth of
 - **a)** the circuit constructed in Example 2 for majority voting among three people.
 - **b**) the circuit constructed in Example 3 for a light controlled by two switches.
 - c) the half adder shown in Figure 8.
 - **d)** the full adder shown in Figure 9.

12.4

Minimization of Circuits

12.4.1 Introduction

The efficiency of a combinational circuit depends on the number and arrangement of its gates. The process of designing a combinational circuit begins with the table specifying the output for each combination of input values. We can always use the sum-of-products expansion of a circuit to find a set of logic gates that will implement this circuit. However, the sum-of-products expansion may contain many more terms than are necessary. Terms in a sum-of-products expansion that differ in just one variable, so that in one term this variable occurs and in the other term the complement of this variable occurs, can be combined. For instance, consider the circuit that has

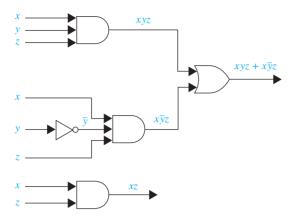


FIGURE 1 Two circuits with the same output.

output 1 if and only if x = y = z = 1 or x = z = 1 and y = 0. The sum-of-products expansion of this circuit is $xyz + x\overline{y}z$. The two products in this expansion differ in exactly one variable, namely, y. They can be combined as

$$xyz + x\overline{y}z = (y + \overline{y})(xz)$$
$$= 1 \cdot (xz)$$
$$= xz.$$

Hence, xz is a Boolean expression with fewer operators that represents the circuit. We show two different implementations of this circuit in Figure 1. The second circuit uses only one gate, whereas the first circuit uses three gates and an inverter.

This example shows that combining terms in the sum-of-products expansion of a circuit leads to a simpler expression for the circuit. We will describe two procedures that simplify sum-of-products expansions.

The goal of both procedures is to produce Boolean sums of Boolean products that represent a Boolean function with the fewest products of literals such that these products contain the fewest literals possible among all sums of products that represent a Boolean function. Finding such a sum of products is called **minimization of the Boolean function**. Minimizing a Boolean function makes it possible to construct a circuit for this function that uses the fewest gates and fewest inputs to the AND gates and OR gates in the circuit, among all circuits for the Boolean expression we are minimizing.

Until the early 1960s logic gates were individual components. To reduce costs it was important to use the fewest gates to produce a desired output. However, in the mid-1960s, integrated circuit technology was developed that made it possible to combine gates on a single chip. Even though it is now possible to build increasingly complex integrated circuits on chips at low cost, minimization of Boolean functions remains important.

Reducing the number of gates on a chip can lead to a more reliable circuit and can reduce the cost to produce the chip. Also, minimization makes it possible to fit more circuits on the same chip. Furthermore, minimization reduces the number of inputs to gates in a circuit. This reduces the time used by a circuit to compute its output. Moreover, the number of inputs to a gate may be limited because of the particular technology used to build logic gates.

The first procedure we will introduce, known as Karnaugh maps (or K-maps), was designed in the 1950s to help minimize circuits by hand. K-maps are useful in minimizing circuits with up to six variables, although they become rather complex even for five or six variables. The second procedure we will describe, the Quine–McCluskey method, was invented in the 1960s. It automates the process of minimizing combinatorial circuits and can be implemented as a computer program.

COMPLEXITY OF BOOLEAN FUNCTION MINIMIZATION Unfortunately, minimizing Boolean functions with many variables is a computationally intensive problem. It has been shown that this problem is an NP-complete problem (see Section 3.3 and [Ka93]), so the existence of a polynomial-time algorithm for minimizing Boolean circuits is unlikely. The Quine–McCluskey method has exponential complexity. In practice, it can be used only when the number of literals does not exceed ten. Since the 1970s a number of newer algorithms have been developed for minimizing combinatorial circuits (see [Ha93] and [KaBe04]). However, with the best algorithms yet devised, only circuits with no more than 25 variables can be minimized. Also, heuristic (or rule-of-thumb) methods can be used to substantially simplify, but not necessarily minimize, Boolean expressions with a larger number of literals.

12.4.2 Karnaugh Maps

Links >

To reduce the number of terms in a Boolean expression representing a circuit, it is necessary to find terms to combine. There is a graphical method, called a **Karnaugh map** or **K-map**, for finding terms to combine for Boolean functions involving a relatively small number of variables. The method we will describe was introduced by Maurice Karnaugh in 1953. His method is based on earlier work by E. W. Veitch. (This method is usually applied only when the function involves six or fewer variables.) K-maps give us a visual method for simplifying sum-of-products expansions; they are not suited for mechanizing this process. We will first illustrate how K-maps are used to simplify expansions of Boolean functions in two variables. We will continue by showing how K-maps can be used to minimize Boolean functions in three variables and then in four variables. Then we will describe the concepts that can be used to extend K-maps to minimize Boolean functions in more than four variables.

There are four possible minterms in the sum-of-products expansion of a Boolean function in the two variables x and y. A K-map for a Boolean function in these two variables consists of four cells, where a 1 is placed in the cell representing a minterm if this minterm is present in the expansion. Cells are said to be **adjacent** if the minterms that they represent differ in exactly one literal. For instance, the cell representing $\overline{x}y$ is adjacent to the cells representing xy and $\overline{x}\overline{y}$. The four cells and the terms that they represent are shown in Figure 2.



FIGURE 2 K-maps in two variables.

EXAMPLE 1

Find the K-maps for (a) $xy + \overline{x}y$, (b) $x\overline{y} + \overline{x}y$, and (c) $x\overline{y} + \overline{x}y + \overline{x}\overline{y}$.

Solution: We include a 1 in a cell when the minterm represented by this cell is present in the sum-of-products expansion. The three K-maps are shown in Figure 3.


We can identify minterms that can be combined from the K-map. Whenever there are 1s in two adjacent cells in the K-map, the minterms represented by these cells can be combined into a product involving just one of the variables. For instance, $x\overline{y}$ and $\overline{x}\overline{y}$ are represented by adjacent cells and can be combined into \overline{y} , because $x\overline{y} + \overline{x}\overline{y} = (x + \overline{x})\overline{y} = \overline{y}$. Moreover, if 1s are in all four cells, the four minterms can be combined into one term, namely, the Boolean expression 1 that involves none of the variables. We circle blocks of cells in the K-map that represent minterms that can be combined and then find the corresponding sum of products. The goal is to identify

Links



Courtesy of Maurice Karnaugh

MAURICE KARNAUGH (BORN 1924) Maurice Karnaugh, born in New York City, received his B.S. from the City College of New York and his M.S. and Ph.D. from Yale University. He was a member of the technical staff at Bell Laboratories from 1952 until 1966 and Manager of Research and Development at the Federal Systems Division of AT&T from 1966 to 1970. In 1970 he joined IBM as a member of the research staff. Karnaugh has made fundamental contributions to the application of digital techniques in both computing and telecommunications. His current interests include knowledge-based systems in computers and heuristic search methods.

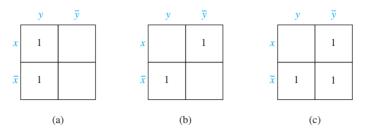

K-maps for the sum-of-products expansions in Example 1. FIGURE 3

the largest possible blocks, and to cover all the 1s with the fewest blocks using the largest blocks first and always using the largest possible blocks.

EXAMPLE 2 Simplify the sum-of-products expansions given in Example 1.

Solution: The grouping of minterms is shown in Figure 4 using the K-maps for these expansions. Minimal expansions for these sums-of-products are (a) y, (b) $x\overline{y} + \overline{x}y$, and (c) $\overline{x} + \overline{y}$.


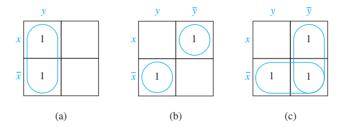


FIGURE 4 Simplifying the sum-of-products expansions from Example 2.

A K-map in three variables is a rectangle divided into eight cells. The cells represent the eight possible minterms in three variables. Two cells are said to be adjacent if the minterms that they represent differ in exactly one literal. One of the ways to form a K-map in three variables is shown in Figure 5(a). This K-map can be thought of as lying on a cylinder, as shown in Figure 5(b). On the cylinder, two cells have a common border if and only if they are adjacent.

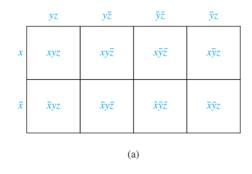

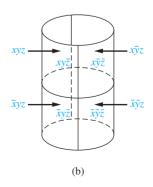


FIGURE 5 K-maps in three variables.

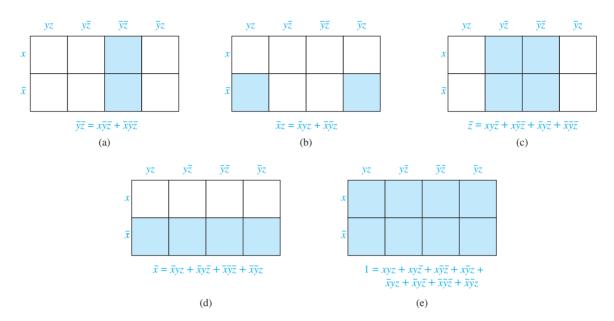


FIGURE 6 Blocks in K-maps in three variables.

To simplify a sum-of-products expansion in three variables, we use the K-map to identify blocks of minterms that can be combined. Blocks of two adjacent cells represent pairs of minterms that can be combined into a product of two literals; 2×2 and 4×1 blocks of cells represent minterms that can be combined into a single literal; and the block of all eight cells represents a product of no literals, namely, the function 1. In Figure 6, 1×2 , 2×1 , 2×2 , 4×1 , and 4×2 blocks and the products they represent are shown.

The product of literals corresponding to a block of all 1s in the K-map is called an **implicant** of the function being minimized. It is called a **prime implicant** if this block of 1s is not contained in a larger block of 1s representing the product of fewer literals than in this product.

The goal is to identify the largest possible blocks in the map and cover all the 1s in the map with the least number of blocks, using the largest blocks first. The largest possible blocks are always chosen, but we must always choose a block if it is the only block of 1s covering a 1 in the K-map. Such a block represents an **essential prime implicant**. By covering all the 1s in the map with blocks corresponding to prime implicants we can express the sum of products as a sum of prime implicants. Note that there may be more than one way to cover all the 1s using the least number of blocks.

Example 3 illustrates how K-maps in three variables are used.

EXAMPLE 3 Use K-maps to minimize these sum-of-products expansions.

- (a) $xy\overline{z} + x\overline{y}\overline{z} + \overline{x}yz + \overline{x}\overline{y}\overline{z}$
- (b) $x\overline{y}z + x\overline{y}\overline{z} + \overline{x}yz + \overline{x}\overline{y}z + \overline{x}\overline{y}\overline{z}$
- (c) $xyz + xy\overline{z} + x\overline{y}z + x\overline{y}\overline{z} + \overline{x}yz + \overline{x}\overline{y}z + \overline{x}\overline{y}\overline{z}$
- (d) $xy\overline{z} + x\overline{y}\overline{z} + \overline{x}\overline{y}z + \overline{x}\overline{y}\overline{z}$

Solution: The K-maps for these sum-of-products expansions are shown in Figure 7. The grouping of blocks shows that minimal expansions into Boolean sums of Boolean products are (a) $x\overline{z} + \overline{y}\overline{z} + \overline{x}yz$, (b) $\overline{y} + \overline{x}z$, (c) $x + \overline{y} + z$, and (d) $x\overline{z} + \overline{x}\overline{y}$. In part (d) note that the prime implicants $x\overline{z}$ and $\overline{x}\overline{y}$ are essential prime implicants, but the prime implicant $\overline{y}\overline{z}$ is a

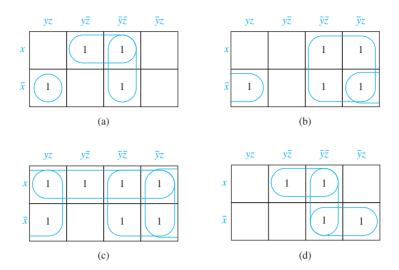


FIGURE 7 Using K-maps in three variables.

prime implicant that is not essential, because the cells it covers are covered by the other two prime implicants.

A K-map in four variables is a square that is divided into 16 cells. The cells represent the 16 possible minterms in four variables. One of the ways to form a K-map in four variables is shown in Figure 8.

Two cells are adjacent if and only if the minterms they represent differ in one literal. Consequently, each cell is adjacent to four other cells. The K-map of a sum-of-products expansion in four variables can be thought of as lying on a torus, so that adjacent cells have a common boundary (see Exercise 28). The simplification of a sum-of-products expansion in four variables is carried out by identifying those blocks of 2, 4, 8, or 16 cells that represent minterms that can be combined. Each cell representing a minterm must either be used to form a product using fewer literals, or be included in the expansion. In Figure 9 some examples of blocks that represent products of three literals, products of two literals, and a single literal are illustrated.

As is the case in K-maps in two and three variables, the goal is to identify the largest blocks of 1s in the map that correspond to the prime implicants and to cover all the 1s using the fewest blocks needed, using the largest blocks first. The largest possible blocks are always used. Example 4 illustrates how K-maps in four variables are used.

	yz	$y\overline{z}$	$\bar{y}\bar{z}$	$\bar{y}z$
wx	wxyz	wxy z	wxÿz̄	wx y z
$w\bar{x}$	w x yz	w x y z	wx̄ȳz̄	wx̄ȳz
$\bar{w}\bar{x}$	$\bar{w}\bar{x}yz$	$\overline{w}\overline{x}y\overline{z}$	<i>w</i> xyz	w̄xȳz
$\bar{w}x$	w <i>xyz</i>	w̄xyz̄	<i>w</i> xyz	ww.yz

FIGURE 8 K-maps in four variables.

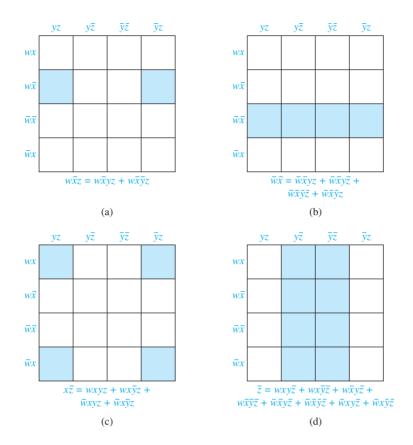


FIGURE 9 Blocks in K-maps in four variables.

EXAMPLE 4 Use K-maps to simplify these sum-of-products expansions.

```
(a) wxyz + wxyz + wxy z + wxyz + wx yz + wx yz + wx yz + wxyz +
```

Solution: The K-maps for these expansions are shown in Figure 10. Using the blocks shown leads to the sum of products (a) $wyz + wx\overline{z} + w\overline{x}y + \overline{w}xy + \overline{w}xyz$, (b) $\overline{y}\overline{z} + wxy + \overline{x}\overline{z}$, and (c) $\overline{z} + \overline{w}x + w\overline{x}y$. The reader should determine whether there are other choices of blocks in each part that lead to different sums of products representing these Boolean functions.

K-maps can realistically be used to minimize Boolean functions with five or six variables, but beyond that, they are rarely used because they become extremely complicated. However, the concepts used in K-maps play an important role in newer algorithms. Furthermore, mastering these concepts helps you understand these newer algorithms and the computer-aided design (CAD) programs that implement them. As we develop these concepts, we will be able to illustrate them by referring back to our discussion of minimization of Boolean functions in three and in four variables.

The K-maps we used to minimize Boolean functions in two, three, and four variables are built using 2×2 , 2×4 , and 4×4 rectangles, respectively. Furthermore, corresponding cells in

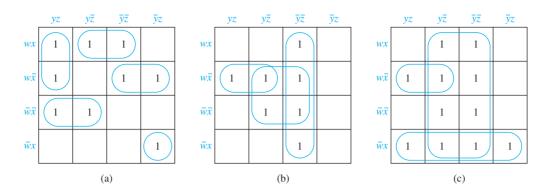


FIGURE 10 Using K-maps in four variables.

the top row and bottom row and in the leftmost column and rightmost column in each of these cases are considered adjacent because they represent minterms differing in only one literal. We can build K-maps for minimizing Boolean functions in more than four variables in a similar way. We use a rectangle containing $2^{\lfloor n/2 \rfloor}$ rows and $2^{\lceil n/2 \rceil}$ columns, (These K-maps contain 2^n cells because $\lceil n/2 \rceil + \lceil n/2 \rceil = n$.) The rows and columns need to be positioned so that the cells representing minterms differing in just one literal are adjacent or are considered adjacent by specifying additional adjacencies of rows and columns. To help (but not entirely) achieve this, the rows and columns of a K-map are arranged using Gray codes (see Section 10.5), where we associate bit strings and products by specifying that a 1 corresponds to the appearance of a variable and a 0 with the appearance of its complement. For example, in a 10-dimensional K-map, the Gray code 01110 used to label a row corresponds to the product $\bar{x}_1 x_2 x_3 x_4 \bar{x}_5$.

EXAMPLE 5

The K-maps we used to minimize Boolean functions with four variables have four rows and four columns. Both the rows and the columns are arranged using the Gray code 11,10,00,01. The rows represent products wx, $w\overline{x}$, $\overline{w}\overline{x}$, and $\overline{w}x$, respectively, and the columns correspond to the products yz, $y\overline{z}$, $\overline{y}\overline{z}$, and $\overline{y}z$, respectively. Using Gray codes and considering cells adjacent in the first and last rows and in the first and last columns, we ensured that minterms that differ in only one variable are always adjacent.

EXAMPLE 6

To minimize Boolean functions in five variables we use K-maps with $2^3 = 8$ columns and $2^2 = 4$ rows. We label the four rows using the Gray code 11,10,00,01, corresponding to $x_1x_2, x_1\bar{x}_2, \bar{x}_1\bar{x}_2$, and \bar{x}_1x_2 , respectively. We label the eight columns using the Gray code 111,110,100,101,001,000,010,011 corresponding to the terms $x_3x_4x_5$, $x_3x_4\bar{x}_5$, $x_3\bar{x}_4\bar{x}_5$, $x_3\bar{x}_4x_5$, $\bar{x}_3\bar{x}_4x_5$, $\bar{x}_3\bar{x}_4\bar{x}_5$, $\bar{x}_3x_4\bar{x}_5$, and $\bar{x}_3x_4x_5$, respectively. Using Gray codes to label columns and rows ensures that the minterms represented by adjacent cells differ in only one variable. However, to make sure all cells representing products that differ in only one variable are considered adjacent, we consider cells in the top and bottom rows to be adjacent, as well as cells in the first and eighth columns, the first and fourth columns, the second and seventh columns, the third and sixth columns, and the fifth and eighth columns (as the reader should verify).

To use a K-map to minimize a Boolean function in n variables, we first draw a K-map of the appropriate size. We place 1s in all cells corresponding to minterms in the sum-of-products expansion of this function. We then identify all prime implicants of the Boolean function. To do this we look for the blocks consisting of 2^k clustered cells all containing a 1, where $1 \le k \le n$. These blocks correspond to the product of n-k literals. (Exercise 33 asks the reader to verify this.) Furthermore, a block of 2^k cells each containing a 1 not contained in a block of 2^{k+1} cells each containing a 1 represents a prime implicant. The reason that this implicant is a prime implicant is that no product obtained by deleting a literal is also represented by a block of cells all containing 1s.

EXAMPLE 7

A block of eight cells representing a product of two literals in a K-map for minimizing Boolean functions in five variables all containing 1s is a prime implicant if it is not contained in a larger block of 16 cells all containing 1s representing a single literal.

Once all prime implicants have been identified, the goal is to find the smallest possible subset of these prime implicants with the property that the cells representing these prime implicants cover all the cells containing a 1 in the K-map. We begin by selecting the essential prime implicants because each of these is represented by a block that covers a cell containing a 1 that is not covered by any other prime implicant. We add additional prime implicants to ensure that all 1s in the K-map are covered. When the number of variables is large, this last step can become exceedingly complicated.

12.4.3 **Don't Care Conditions**

Links

In some circuits we care only about the output for some combinations of input values, because other combinations of input values are not possible or never occur. This gives us freedom in producing a simple circuit with the desired output because the output values for all those combinations that never occur can be arbitrarily chosen. The values of the function for these combinations are called *don't care* conditions. A d is used in a K-map to mark those combinations of values of the variables for which the function can be arbitrarily assigned. In the minimization process we can assign 1s as values to those combinations of the input values that lead to the largest blocks in the K-map. This is illustrated in Example 8.

EXAMPLE 8

One way to code decimal expansions using bits is to use the four bits of the binary expansion of each digit in the decimal expansion. For instance, 873 is encoded as 100001110011. This encoding of a decimal expansion is called a binary coded decimal expansion. Because there are 16 blocks of four bits and only 10 decimal digits, there are six combinations of four bits that are not used to encode digits. Suppose that a circuit is to be built that produces an output of 1 if the decimal digit is 5 or greater and an output of 0 if the decimal digit is less than 5. How can this circuit be simply built using OR gates, AND gates, and inverters?

Solution: Let F(w, x, y, z) denote the output of the circuit, where wxyz is a binary expansion of a decimal digit. The values of F are shown in Table 1. The K-map for F, with ds in the

TABLE 1								
Digit	w	х	у	z	F			
0	0	0	0	0	0			
1	0	0	0	1	0			
2	0	0	1	0	0			
3	0	0	1	1	0			
4	0	1	0	0	0			
5	0	1	0	1	1			
6	0	1	1	0	1			
7	0	1	1	1	1			
8	1	0	0	0	1			
9	1	0	0	1	1			

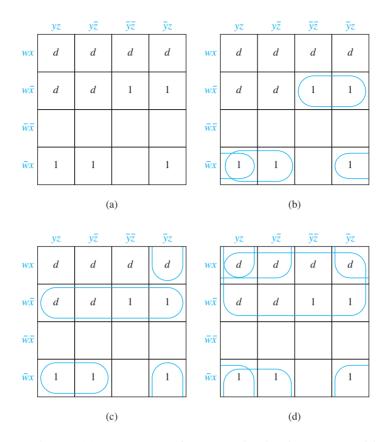


FIGURE 11 The K-map for F showing its don't care positions.

don't care positions, is shown in Figure 11(a). We can either include or exclude squares with ds from blocks. This gives us many possible choices for the blocks. For example, excluding all squares with ds and forming blocks, as shown in Figure 11(b), produces the expression $w\bar{x}\,\bar{y} + \bar{w}xy + \bar{w}xz$. Including some of the ds and excluding others and forming blocks, as shown in Figure 11(c), produces the expression $w\bar{x} + \bar{w}xy + x\bar{y}z$. Finally, including all the ds and using the blocks shown in Figure 11(d) produces the simplest sum-of-products expansion possible, namely, F(x, y, z) = w + xy + xz.

The Quine-McCluskey Method

Links

We have seen that K-maps can be used to produce minimal expansions of Boolean functions as Boolean sums of Boolean products. However, K-maps are awkward to use when there are

Links



©Stanford University News

EDWARD J. McCLUSKEY (1929-2016) Edward McCluskey attended Bowdoin College and M.I.T., where he received his doctorate in electrical engineering in 1956. He joined Bell Telephone Laboratories in 1955, remaining there until 1959. McCluskey was professor of electrical engineering at Princeton University from 1959 until 1966, also serving as director of the Computer Center at Princeton from 1961 to 1966. In 1967 he took a position as professor of computer science and electrical engineering at Stanford University, where he also served as director of the Digital Systems Laboratory from 1969 to 1978. McCluskey worked in a variety of areas in computer science, including fault-tolerant computing, computer architecture, testing, and logic design. He was the director of the Center for Reliable Computing at Stanford University and an ACM Fellow.

TABLE 2							
Minterm	Bit String	Number of 1s					
xyz	111	3					
$x\overline{y}z$	101	2					
$\frac{x\overline{y}z}{\overline{x}yz}$	011	2					
$\overline{x}\overline{y}z$	001	1					
$\bar{x}\bar{y}\bar{z}$	000	0					

more than four variables. Furthermore, the use of K-maps relies on visual inspection to identify terms to group. For these reasons there is a need for a procedure for simplifying sum-of-products expansions that can be mechanized. The Quine–McCluskey method is such a procedure. It can be used for Boolean functions in any number of variables. It was developed in the 1950s by W. V. Quine and E. J. McCluskey, Jr. Basically, the Quine–McCluskey method consists of two parts. The first part finds those terms that are candidates for inclusion in a minimal expansion as a Boolean sum of Boolean products. The second part determines which of these terms to actually use. We will use Example 9 to illustrate how, by successively combining implicants into implicants with one fewer literal, this procedure works.

EXAMPLE 9

We will show how the Quine-McCluskey method can be used to find a minimal expansion equivalent to

$$xyz + x\overline{y}z + \overline{x}yz + \overline{x}\overline{y}z + \overline{x}\overline{y}\overline{z}$$
.

We will represent the minterms in this expansion by bit strings. The first bit will be 1 if x occurs and 0 if \overline{x} occurs. The second bit will be 1 if y occurs and 0 if \overline{y} occurs. The third bit will be 1 if z occurs and 0 if \overline{z} occurs. We then group these terms according to the number of 1s in the corresponding bit strings. This information is shown in Table 2.

Minterms that can be combined are those that differ in exactly one literal. Hence, two terms that can be combined differ by exactly one in the number of 1s in the bit strings that represent them. When two minterms are combined into a product, this product contains two literals. A product in two literals is represented using a dash to denote the variable that does not occur. For instance, the minterms $x\bar{y}z$ and $\bar{x}\bar{y}z$, represented by bit strings 101 and 001, can be combined into $\bar{y}z$, represented by the string -01. All pairs of minterms that can be combined and the product formed from these combinations are shown in Table 3.

Next, all pairs of products of two literals that can be combined are combined into one literal. Two such products can be combined if they contain literals for the same two variables, and literals for only one of the two variables differ. In terms of the strings representing the

TABLE 3									
		Step 1			Step 2				
	Term	Bit String		Term	String		Term	String	
1	xyz	111	(1,2)	xz	1–1	(1,2,3,4)	z	1	
2	$x\overline{y}z$	101	(1,3)	yz	-11				
3	$\bar{x}yz$	011	(2,4)	$\overline{y}z$	-01				
4	$\bar{x}\bar{y}z$	001	(3,4)	$\overline{x}z$	0–1				
5	$\overline{x}\overline{y}\overline{z}$	000	(4,5)	$\bar{x}\bar{y}$	00–				

TABLE 4							
	xyz	xyz	$\bar{x}yz$	$\bar{x}\bar{y}z$	$\bar{x}\bar{y}\bar{z}$		
z	X	X	X	X			
$\bar{x}\bar{y}$				X	X		

products, these strings must have a dash in the same position and must differ in exactly one of the other two slots. We can combine the products yz and $\overline{y}z$, represented by the strings -11and -01, into z, represented by the string -1. We show all the combinations of terms that can be formed in this way in Table 3.

In Table 3 we also indicate which terms have been used to form products with fewer literals; these terms will not be needed in a minimal expansion. The next step is to identify a minimal set of products needed to represent the Boolean function. We begin with all those products that were not used to construct products with fewer literals. Next, we form Table 4, which has a row for each candidate product formed by combining original terms, and a column for each original term; and we put an X in a position if the original term in the sum-of-products expansion was used to form this candidate product. In this case, we say that the candidate product covers the original minterm. We need to include at least one product that covers each of the original minterms. Consequently, whenever there is only one X in a column in the table, the product corresponding to the row this X is in must be used. From Table 4 we see that both z and $\bar{x}\bar{y}$ are needed. Hence, the final answer is $z + \overline{x} \overline{y}$.

As was illustrated in Example 9, the Quine–McCluskey method uses this sequence of steps to simplify a sum-of-products expression.



- 1. Express each minterm in n variables by a bit string of length n with a 1 in the ith position if x_i occurs and a 0 in this position if \overline{x}_i occurs.
- 2. Group the bit strings according to the number of 1s in them.
- 3. Determine all products in n-1 variables that can be formed by taking the Boolean sum of minterms in the expansion. Minterms that can be combined are represented by bit strings that differ in exactly one position. Represent these products in n-1 variables with strings that have a 1 in the *i*th position if x_i occurs in the product, a 0 in this position if \bar{x}_i occurs, and a dash in this position if there is no literal involving x_i in the product.



WILLARD VAN ORMAN QUINE (1908–2000) Willard Quine, born in Akron, Ohio, attended Oberlin College and later Harvard University, where he received his Ph.D. in philosophy in 1932. He became a Junior Fellow at Harvard in 1933 and was appointed to a position on the faculty there in 1936. He remained at Harvard his entire professional life, except for World War II, when he worked for the U.S. Navy decrypting messages from German submarines. Quine was always interested in algorithms, but not in hardware. He arrived at his discovery of what is now called the Quine-McCluskey method as a device for teaching mathematical logic, rather than as a method for simplifying switching circuits. Quine was one of the most famous philosophers of the twentieth century. He made fundamental contributions to the theory of knowledge, mathematical logic and set theory, and the philosophies of logic and language. His books, including New Foundations of Mathematical Logic published in 1937 and Word and Object published in 1960, have had a profound impact. Quine

retired from Harvard in 1978 but continued to commute from his home in Beacon Hill to his office there. He used the 1927 Remington typewriter on which he prepared his doctoral thesis for his entire life. He even had an operation performed on this machine to add a few special symbols, removing the second period, the second comma, and the question mark. When asked whether he missed the question mark, he replied, "Well, you see, I deal in certainties." There is even a word quine, defined in the New Hacker's Dictionary as a program that generates a copy of its own source code as its complete output. Producing the shortest possible quine in a given programming language is a popular puzzle for hackers.

- 4. Determine all products in n-2 variables that can be formed by taking the Boolean sum of the products in n-1 variables found in the previous step. Products in n-1 variables that can be combined are represented by bit strings that have a dash in the same position and differ in exactly one position.
- 5. Continue combining Boolean products into products in fewer variables as long as possible.
- 6. Find all the Boolean products that arose that were not used to form a Boolean product in one fewer literal.
- 7. Find the smallest set of these Boolean products such that the sum of these products represents the Boolean function. This is done by forming a table showing which minterms are covered by which products. Every minterm must be covered by at least one product. The first step in using this table is to find all essential prime implicants. Each essential prime implicant must be included because it is the only prime implicant that covers one of the minterms. Once we have found essential prime implicants, we can simplify the table by eliminating the rows for minterms covered by these prime implicants. Furthermore, we can eliminate any prime implicants that cover a subset of minterms covered by another prime implicant (as the reader should verify). Moreover, we can eliminate from the table the row for a minterm if there is another minterm that is covered by a subset of the prime implicants that cover this minterm. This process of identifying essential prime implicants that must be included, followed by eliminating redundant prime implicants and identifying minterms that can be ignored, is iterated until the table does not change. At this point we use a backtracking procedure to find the optimal solution where we add prime implicants to the cover to find possible solutions, which we compare to the best solution found so far at each step.

A final example will illustrate how this procedure is used to simplify a sum-of-products expansion in four variables.

EXAMPLE 10

Use the Quine–McCluskey method to simplify the sum-of-products expansion $wxy\overline{z} + w\overline{x}yz + w\overline{x}y\overline{z} + \overline{w}x\overline{y}z + \overline{w}\overline{x}yz + \overline$

Solution: We first represent the minterms by bit strings and then group these terms together according to the number of 1s in the bit strings. This is shown in Table 5. All the Boolean products that can be formed by taking Boolean sums of these products are shown in Table 6.

The only products that were not used to form products in fewer variables are \overline{wz} , $wy\overline{z}$, $w\overline{xy}$, and $\overline{x}yz$. In Table 7 we show the minterms covered by each of these products. To cover these minterms we must include $\overline{w}z$ and $wy\overline{z}$, because these products are the only products that cover $\overline{w}xyz$ and $\overline{w}xy\overline{z}$, respectively. Once these two products are included, we see that only one of the two products left is needed. Consequently, we can take either $\overline{w}z + wy\overline{z} + w\overline{x}y$ or $\overline{w}z + wy\overline{z} + \overline{x}yz$ as the final answer.

TABLE 5						
Term	Bit String	Number of 1s				
$wxy\overline{z}$	1110	3				
$w\overline{x}yz$	1011	3				
$\overline{w}xyz$	0111	3				
$w\overline{x}y\overline{z}$	1010	2				
$\overline{w}x\overline{y}z$	0101	2				
$\overline{w}\overline{x}yz$	0011	2				
$\overline{w}\overline{x}\overline{y}z$	0001	1				

TABLE 6								
			Step 1			Step 2		
	Term	Bit String		Term	String		Term	String
1	$wxy\overline{z}$	1110	(1,4)	wy z	1–10	(3,5,6,7)	$\overline{w}z$	0 – –1
2	$w\overline{x}yz$	1011	(2,4)	$w\overline{x}y$	101-			
3	$\overline{w}xyz$	0111	(2,6)	$\overline{x}yz$	-011			
4	$w\overline{x}y\overline{z}$	1010	(3,5)	$\overline{w}xz$	01–1			
5	$\overline{w}x\overline{y}z$	0101	(3,6)	$\overline{w}yz$	0–11			
6	$\overline{w}\overline{x}yz$	0011	(5,7)	$\overline{w}\overline{y}z$	0–01			
7	$\overline{w}\overline{x}\overline{y}z$	0001	(6,7)	$\overline{w}\overline{x}z$	00–1			

TABLE 7								
	wxyz	w x yz	— wxyz	w x yz	wxyz	$\overline{w} \overline{x} yz$	$\overline{w} \overline{x} \overline{y} z$	
$\overline{w}z$			X		X	X	X	
wy z	X			X				
$w\overline{x}y$		X		X				
$\overline{x}yz$		X				X		

Exercises

- 1. a) Draw a K-map for a function in two variables and put a 1 in the cell representing $\overline{x}y$.
 - b) What are the minterms represented by cells adjacent to this cell?
- 2. Find the sum-of-products expansions represented by each of these K-maps.









- 3. Draw the K-maps of these sum-of-products expansions in two variables.
 - a) $x\overline{y}$

- **b)** $xy + \overline{x}\overline{y}$
- c) $xy + x\overline{y} + \overline{x}y + \overline{x}\overline{y}$
- 4. Use a K-map to find a minimal expansion as a Boolean sum of Boolean products of each of these functions of the Boolean variables x and y.
 - a) $\bar{x}y + \bar{x}\bar{y}$
 - **b**) $xy + x\overline{y}$
 - c) $xy + x\overline{y} + \overline{x}y + \overline{x}\overline{y}$

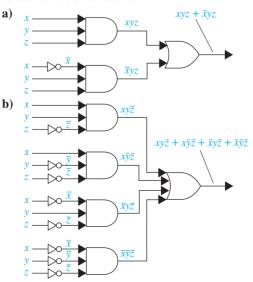- 5. a) Draw a K-map for a function in three variables. Put a 1 in the cell that represents $\bar{x}y\bar{z}$.
 - b) Which minterms are represented by cells adjacent to this cell?
- **6.** Use K-maps to find simpler circuits with the same output as each of the circuits shown.



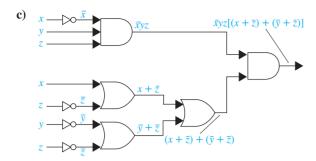

- 7. Draw the K-maps of these sum-of-products expansions in three variables.
 - a) $x\bar{y}\bar{z}$

- **b)** $\bar{x}yz + \bar{x}\bar{y}\bar{z}$
- c) $xyz + xy\overline{z} + \overline{x}y\overline{z} + \overline{x}\overline{y}z$
- **8.** Construct a K-map for $F(x, y, z) = xz + yz + xy\overline{z}$. Use this K-map to find the implicants, prime implicants, and essential prime implicants of F(x, y, z).
- **9.** Construct a K-map for $F(x, y, z) = x\overline{z} + xyz + y\overline{z}$. Use this K-map to find the implicants, prime implicants, and essential prime implicants of F(x, y, z).
- 10. Draw the 3-cube Q_3 and label each vertex with the minterm in the Boolean variables x, y, and z associated with the bit string represented by this vertex. For each literal in these variables indicate the 2-cube Q_2 that is a subgraph of Q_3 and represents this literal.
- 11. Draw the 4-cube Q_4 and label each vertex with the minterm in the Boolean variables w, x, y, and z associated with the bit string represented by this vertex. For each literal in these variables, indicate which 3-cube Q_3 that is a subgraph of Q_4 represents this literal. Indicate which 2-cube Q_2 that is a subgraph of Q_4 represents the products wz, $\overline{x}y$, and $\overline{y}\overline{z}$.
- **12.** Use a K-map to find a minimal expansion as a Boolean sum of Boolean products of each of these functions in the variables x, y, and z.
 - a) $\bar{x}yz + \bar{x}\bar{y}z$
 - **b)** $xyz + xy\overline{z} + \overline{x}yz + \overline{x}y\overline{z}$
 - c) $xy\overline{z} + x\overline{y}z + x\overline{y}\overline{z} + \overline{x}yz + \overline{x}\overline{y}z$
 - **d)** $xyz + x\overline{y}z + x\overline{y}\overline{z} + \overline{x}yz + \overline{x}y\overline{z} + \overline{x}\overline{y}\overline{z}$
- 13. a) Draw a K-map for a function in four variables. Put a 1 in the cell that represents $\overline{w}xy\overline{z}$.
 - b) Which minterms are represented by cells adjacent to
- 14. Use a K-map to find a minimal expansion as a Boolean sum of Boolean products of each of these functions in the variables w, x, y, and z.
 - a) $wxyz + wx\overline{y}z + wx\overline{y}\overline{z} + w\overline{x}y\overline{z} + w\overline{x}\overline{y}z$
 - **b)** $wxy\overline{z} + wx\overline{y}z + w\overline{x}yz + \overline{w}x\overline{y}z + \overline{w}\overline{x}y\overline{z} + \overline{w}\overline{x}\overline{y}z$
 - c) $wxyz + wxy\overline{z} + wx\overline{y}z + wx\overline{$ $\overline{w}x\overline{y}z + \overline{w}\overline{x}y\overline{z} + \overline{w}\overline{x}\overline{y}z$
 - d) $wxyz + wxy\overline{z} + wx\overline{y}z + w\overline{x}yz + w\overline{x}y\overline{z} +$ $\overline{w}xyz + \overline{w}\overline{x}yz + \overline{w}\overline{x}y\overline{z} + \overline{w}\overline{x}\overline{y}z$

- 15. Find the cells in a K-map for Boolean functions with five variables that correspond to each of these products.
 - **a**) $x_1 x_2 x_3 x_4$
- **b**) $\bar{x}_1 x_3 x_5$

- **d**) $\overline{x}_3\overline{x}_4$

- 16. How many cells in a K-map for Boolean functions with six variables are needed to represent x_1 , \bar{x}_1x_6 , $\overline{x}_1 x_2 \overline{x}_6$, $x_2 x_3 x_4 x_5$, and $x_1 \overline{x}_2 x_4 \overline{x}_5$, respectively?
- 17. a) How many cells does a K-map in six variables have?
 - b) How many cells are adjacent to a given cell in a Kmap in six variables?
- 18. Show that cells in a K-map for Boolean functions in five variables represent minterms that differ in exactly one literal if and only if they are adjacent or are in cells that become adjacent when the top and bottom rows and cells in the first and eighth columns, the first and fourth columns, the second and seventh columns, the third and sixth columns, and the fifth and eighth columns are considered adjacent.
- 19. Which rows and which columns of a 4×16 map for Boolean functions in six variables using the Gray codes 1111, 1110, 1010, 1011, 1001, 1000, 0000, 0001, 0011, 0010, 0110, 0111, 0101, 0100, 1100, 1101 to label the columns and 11, 10, 00, 01 to label the rows need to be considered adjacent so that cells that represent minterms that differ in exactly one literal are considered adjacent?
- *20. Use K-maps to find a minimal expansion as a Boolean sum of Boolean products of Boolean functions that have as input the binary code for each decimal digit and produce as output a 1 if and only if the digit corresponding to the input is
 - a) odd.

- **b)** not divisible by 3.
- c) not 4, 5, or 6.
- *21. Suppose that there are five members on a committee, but that Smith and Jones always vote the opposite of Marcus. Design a circuit that implements majority voting of the committee using this relationship between votes.
 - 22. Use the Quine–McCluskey method to simplify the sumof-products expansions in Example 3.
 - 23. Use the Quine–McCluskey method to simplify the sumof-products expansions in Exercise 12.
- 24. Use the Quine–McCluskey method to simplify the sumof-products expansions in Example 4.
- 25. Use the Ouine–McCluskey method to simplify the sumof-products expansions in Exercise 14.
- *26. Explain how K-maps can be used to simplify product-ofsums expansions in three variables. [Hint: Mark with a 0 all the maxterms in an expansion and combine blocks of maxterms.]
 - 27. Use the method from Exercise 26 to simplify the product- $(x+y+z)(x+y+\overline{z})(x+\overline{y}+\overline{z})$ of-sums expansion $(x + \overline{y} + z)(\overline{x} + y + z).$
- *28. Draw a K-map for the 16 minterms in four Boolean variables on the surface of a torus.

29. Build a circuit using OR gates, AND gates, and inverters that produces an output of 1 if a decimal digit, encoded using a binary coded decimal expansion, is divisible by 3, and an output of 0 otherwise.

In Exercises 30-32 find a minimal sum-of-products expansion, given the K-map shown with don't care conditions indicated with ds.

30.		yz	ӯ	ӯ̄z̄	ӯz
	wx	d	1	d	1
	$w\bar{x}$		d	d	
	$\overline{w}\overline{x}$		d	1	
	$\overline{w}x$		1	d	

31.		yz	ӯz	ӯ̄z̄	ӯz
	wx	1			1
	$w\bar{x}$		d	1	
	$\overline{w}\overline{x}$		1	d	
	$\overline{w}x$	d			d

32.		yz	ӯ	ӯ̄z̄	ӯz
	wx		d	d	1
	$w\bar{x}$	d	d	1	d
	$\overline{w}\overline{x}$				
	$\overline{w}x$	1	1	1	d

33. Show that products of k literals correspond to 2^{n-k} dimensional subcubes of the *n*-cube Q_n , where the vertices of the cube correspond to the minterms represented by the bit strings labeling the vertices, as described in Example 8 of Section 10.2.

Key Terms and Results

TERMS

- **Boolean variable:** a variable that assumes only the values 0 and 1
- \bar{x} (complement of x): an expression with the value 1 when x has the value 0 and the value 0 when x has the value 1
- $x \cdot y$ (or xy) (Boolean product or conjunction of x and y): an expression with the value 1 when both x and y have the value 1 and the value 0 otherwise
- x + y (Boolean sum or disjunction of x and y): an expression with the value 1 when either x or y, or both, has the value 1, and 0 otherwise
- **Boolean expressions:** the expressions obtained recursively by specifying that 0, 1, x_1, \ldots, x_n are Boolean expressions and \overline{E}_1 , $(E_1 + E_2)$, and $(E_1 E_2)$ are Boolean expressions if E_1 and
- dual of a Boolean expression: the expression obtained by interchanging + signs and · signs and interchanging 0s and
- **Boolean function of degree** n**:** a function from B^n to B where $B = \{0, 1\}$
- **Boolean algebra:** a set B with two binary operations \vee and \wedge , elements 0 and 1, and a complementation operator - that satisfies the identity, complement, associative, commutative, and distributive laws

literal of the Boolean variable x: either x or \bar{x}

- **minterm of** x_1, x_2, \dots, x_n : a Boolean product $y_1 y_2 \cdots y_n$, where each y_i is either x_i or \overline{x}_i
- sum-of-products expansion (or disjunctive normal form): the representation of a Boolean function as a disjunction of minterms
- functionally complete: a set of Boolean operators is called functionally complete if every Boolean function can be represented using these operators

- $x \mid v$ (or x NAND v): the expression that has the value 0 when both x and y have the value 1 and the value 1 otherwise
- $x \downarrow y$ (or x NOR y): the expression that has the value 0 when either x or y or both have the value 1 and the value 0 otherwise
- inverter: a device that accepts the value of a Boolean variable as input and produces the complement of the input
- **OR gate:** a device that accepts the values of two or more Boolean variables as input and produces their Boolean sum as output
- **AND gate:** a device that accepts the values of two or more Boolean variables as input and produces their Boolean product as output
- half adder: a circuit that adds two bits, producing a sum bit and a carry bit
- full adder: a circuit that adds two bits and a carry, producing a sum bit and a carry bit
- **K-map for** n **variables:** a rectangle divided into 2^n cells where each cell represents a minterm in the variables
- minimization of a Boolean function: representing a Boolean function as the sum of the fewest products of literals such that these products contain the fewest literals possible among all sums of products that represent this Boolean function
- implicant of a Boolean function: a product of literals with the property that if this product has the value 1, then the value of this Boolean function is 1
- prime implicant of a Boolean function: a product of literals that is an implicant of the Boolean function and no product obtained by deleting a literal is also an implicant of this function
- essential prime implicant of a Boolean function: a prime implicant of the Boolean function that must be included in a minimization of this function
- don't care condition: a combination of input values for a circuit that is not possible or never occurs

RESULTS

The identities for Boolean algebra (see Table 5 in Section 12.1).

An identity between Boolean functions represented by Boolean expressions remains valid when the duals of both sides of the identity are taken.

Every Boolean function can be represented by a sum-of-products expansion.

Each of the sets $\{+, -\}$ and $\{\cdot, -\}$ is functionally complete.

Each of the sets $\{\ \downarrow\ \}$ and $\{\ |\ \}$ is functionally complete.

The use of K-maps to minimize Boolean expressions.

The Quine–McCluskey method for minimizing Boolean expressions.

Review Ouestions

- **1.** Define a Boolean function of degree n.
- 2. How many Boolean functions of degree two are there?
- Give a recursive definition of the set of Boolean expressions.
- **4.** a) What is the dual of a Boolean expression?
 - **b)** What is the duality principle? How can it be used to find new identities involving Boolean expressions?
- **5.** Explain how to construct the sum-of-products expansion of a Boolean function.
- **6. a)** What does it mean for a set of operators to be functionally complete?
 - **b)** Is the set $\{+,\cdot\}$ functionally complete?
 - c) Are there sets of a single operator that are functionally complete?
- 7. Explain how to build a circuit for a light controlled by two switches using OR gates, AND gates, and inverters.
- **8.** Construct a half adder using OR gates, AND gates, and inverters.
- 9. Is there a single type of logic gate that can be used to build all circuits that can be built using OR gates, AND gates, and inverters?

- **10. a)** Explain how K-maps can be used to simplify sum-of-products expansions in three Boolean variables.
 - **b)** Use a K-map to simplify the sum-of-products expansion $xyz + x\overline{y}z + x\overline{y}\overline{z} + \overline{x}yz + \overline{x}\overline{y}\overline{z}$.
- **11. a)** Explain how K-maps can be used to simplify sum-of-products expansions in four Boolean variables.
 - **b)** Use a K-map to simplify the sum-of-products expansion $wxyz + wxy\overline{z} + wx\overline{y}z + wx\overline{y}\overline{z} + w\overline{x}yz + w\overline{x}\overline{y}z + \overline{w}xyz + \overline{w}\overline{x}yz + \overline{w}\overline{x}y\overline{z}$.
- **12. a)** What is a *don't care* condition?
 - **b)** Explain how *don't care* conditions can be used to build a circuit using OR gates, AND gates, and inverters that produces an output of 1 if a decimal digit is 6 or greater, and an output of 0 if this digit is less than 6.
- **13. a)** Explain how to use the Quine–McCluskey method to simplify sum-of-products expansions.
 - **b)** Use this method to simplify $xy\overline{z} + x\overline{y}\overline{z} + \overline{x}y\overline{z} + \overline{x}\overline{y}z + \overline{x}\overline{y}z + \overline{x}\overline{y}z$.

Supplementary Exercises

- 1. For which values of the Boolean variables x, y, and z does
 - **a)** x + y + z = xyz?
 - **b**) x(y + z) = x + yz?
 - c) $\overline{x}\overline{y}\overline{z} = x + y + z$?
- **2.** Let x and y belong to $\{0, 1\}$. Does it necessarily follow that x = y if there exists a value z in $\{0, 1\}$ such that
 - a) xz = yz?
- **b**) x + z = y + z?
- c) $x \oplus z = y \oplus z$?
- **d**) $x \downarrow z = y \downarrow z$?
- **e)** x | z = y | z?

A Boolean function F is called **self-dual** if and only if $F(x_1, ..., x_n) = \overline{F(\overline{x}_1, ..., \overline{x}_n)}$.

- **3.** Which of these functions are self-dual?
 - **a)** F(x, y) = x
- **b)** $F(x, y) = xy + \overline{x}\overline{y}$
- **c**) F(x, y) = x + y
- **d)** $F(x, y) = xy + \overline{x}y$
- **4.** Give an example of a self-dual Boolean function of three variables.

- *5. How many Boolean functions of degree n are self-dual? We define the relation \leq on the set of Boolean functions of degree n so that $F \leq G$, where F and G are Boolean functions if and only if $G(x_1, x_2, \ldots, x_n) = 1$ whenever $F(x_1, x_2, \ldots, x_n) = 1$.
- **6.** Determine whether $F \le G$ or $G \le F$ for the following pairs of functions.
 - **a**) F(x, y) = x, G(x, y) = x + y
 - **b)** F(x, y) = x + y, G(x, y) = xy
 - c) $F(x, y) = \overline{x}$, G(x, y) = x + y
- **7.** Show that if *F* and *G* are Boolean functions of degree *n*, then
 - a) $F \leq F + G$.
- **b**) $FG \leq F$.
- **8.** Show that if F, G, and H are Boolean functions of degree n, then $F + G \le H$ if and only if $F \le H$ and $G \le H$.
- *9. Show that the relation \leq is a partial ordering on the set of Boolean functions of degree n.

- *10. Draw the Hasse diagram for the poset consisting of the set of the 16 Boolean functions of degree two (shown in Table 3 of Section 12.1) with the partial ordering <.
- *11. For each of these equalities either prove it is an identity or find a set of values of the variables for which it does not hold.

a)
$$x | (y | z) = (x | y) | z$$

b)
$$x \downarrow (y \downarrow z) = (x \downarrow y) \downarrow (x \downarrow z)$$

c)
$$x \downarrow (y \mid z) = (x \downarrow y) \mid (x \downarrow z)$$

Define the Boolean operator \odot as follows: $1 \odot 1 = 1$, $1 \odot 0 = 1$ $0, 0 \odot 1 = 0, \text{ and } 0 \odot 0 = 1.$

- 12. Show that $x \odot y = xy + \overline{x} \overline{y}$.
- **13.** Show that $x \odot y = \overline{(x \oplus y)}$.
- 14. Show that each of these identities holds.

a)
$$x \odot x = 1$$

b)
$$x \odot \overline{x} = 0$$

c)
$$x \odot y = y \odot x$$


- **15.** Is it always true that $(x \odot y) \odot z = x \odot (y \odot z)$?
- *16. Determine whether the set $\{\odot\}$ is functionally complete.
- *17. How many of the 16 Boolean functions in two variables x and y can be represented using only the given set of operators, variables x and y, and values 0 and 1?


d)
$$\{\cdot, +\}$$

The notation for an XOR gate, which produces the output $x \oplus y$ from x and y, is as follows:




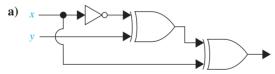18. Determine the output of each of these circuits.




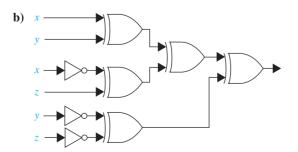

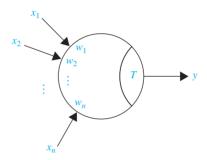- 19. Show how a half adder can be constructed using fewer gates than are used in Figure 8 of Section 12.3 when XOR gates can be used in addition to OR gates, AND gates, and inverters.
- 20. Design a circuit that determines whether three or more of four individuals on a committee vote yes on an issue, where each individual uses a switch for the voting.
- A threshold gate produces an output y that is either 0 or 1 given a set of input values for the Boolean variables x_1, x_2, \dots, x_n . A threshold gate has a **threshold value** T, which is a real number, and weights w_1, w_2, \dots, w_n , each of which is a real number. The output y of the threshold gate is 1 if and only if $w_1x_1 + w_2x_2 + \cdots + w_nx_n \ge T$. The threshold gate with threshold value T and weights w_1, w_2, \ldots, w_n is represented by the following diagram. Threshold gates are useful in modeling in neurophysiology and in artificial intelligence.



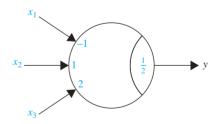21. A threshold gate represents a Boolean function. Find a Boolean expression for the Boolean function represented by this threshold gate.



22. A Boolean function that can be represented by a threshold gate is called a threshold function. Show that each of these functions is a threshold function.

a)
$$F(x) = \overline{x}$$

b)
$$F(x, y) = x + y$$

c)
$$F(x, y) = xy$$

d)
$$F(x, y) = x | y$$

e)
$$F(x, y) = x \downarrow y$$

d)
$$F(x, y) = x \mid y$$

f) $F(x, y, z) = x + yz$

g)
$$F(w, x, y, z) = w + xy + z$$

h)
$$F(w, x, y, z) = wxz + x\overline{y}z$$

- *23. Show that $F(x, y) = x \oplus y$ is not a threshold function.
- *24. Show that F(w, x, y, z) = wx + yz is not a threshold function.

Computer Projects

Write programs with these input and output.

- **1.** Given the values of two Boolean variables x and y, find the values of x + y, xy, $x \oplus y$, $x \mid y$, and $x \downarrow y$.
- **2.** Construct a table listing the set of values of all 256 Boolean functions of degree three.
- **3.** Given the values of a Boolean function in *n* variables, where *n* is a positive integer, construct the sum-of-products expansion of this function.
- **4.** Given the table of values of a Boolean function, express this function using only the operators \cdot and $\overline{\ }$.
- **5.** Given the table of values of a Boolean function, express this function using only the operators + and $\bar{\ }$.
- *6. Given the table of values of a Boolean function, express this function using only the operator |.

- *7. Given the table of values of a Boolean function, express this function using only the operator ↓.
- **8.** Given the table of values of a Boolean function of degree three, construct its K-map.
- **9.** Given the table of values of a Boolean function of degree four, construct its K-map.
- **10. Given the table of values of a Boolean function, use the Quine–McCluskey method to find a minimal sum-of-products representation of this function.
 - **11.** Given a threshold value and a set of weights for a threshold gate and the values of the *n* Boolean variables in the input, determine the output of this gate.
 - **12.** Given a positive integer *n*, construct a random Boolean expression in *n* variables in disjunctive normal form.

Computations and Explorations

Use a computational program or programs you have written to do these exercises.

- 1. Compute the number of Boolean functions of degrees seven, eight, nine, and ten.
- **2.** Construct a table of the Boolean functions of degree three.
- **3.** Construct a table of the Boolean functions of degree four.
- **4.** Express each of the different Boolean expressions in three variables in disjunctive normal form with just the *NAND* operator, using as few *NAND* operators as possible. What is the largest number of *NAND* operators required?
- **5.** Express each of the different Boolean expressions in disjunctive normal form in four variables using just the *NOR*

- operator, with as few *NOR* operators as possible. What is the largest number of *NOR* operators required?
- **6.** Randomly generate 10 different Boolean expressions in four variables and determine the average number of steps required to minimize them using the Quine–McCluskey method.
- Randomly generate 10 different Boolean expressions in five variables and determine the average number of steps required to minimize them using the Quine–McCluskey method.

Writing Projects

Respond to these with essays using outside sources.

- 1. Describe some of the early machines devised to solve problems in logic, such as the Stanhope Demonstrator, Jevons's Logic Machine, and the Marquand Machine.
- **2.** Explain the difference between combinational circuits and sequential circuits. Then explain how *flip-flops* are used to build sequential circuits.
- **3.** Define a *shift register* and discuss how shift registers are used. Show how to build shift registers using flip-flops and logic gates.
- 4. Show how multipliers can be built using logic gates.

- Find out how logic gates are physically constructed. Discuss whether NAND and NOR gates are used in building circuits.
- **6.** Explain how *dependency notation* can be used to describe complicated switching circuits.
- Describe how multiplexers are used to build switching circuits.
- **8.** Explain the advantages of using threshold gates to construct switching circuits. Illustrate this by using threshold gates to construct half and full adders.

- 9. Describe the concept of hazard-free switching circuits and give some of the principles used in designing such
- 10. Explain how to use K-maps to minimize functions of six variables.
- 11. Discuss the ideas used by newer methods for minimizing Boolean functions, such as Espresso. Explain how
- these methods can help solve minimization problems in as many as 25 variables.
- **12.** Describe what is meant by the *functional decomposition* of a Boolean function of n variables and discuss procedures for decomposing Boolean functions into a composition of Boolean functions with fewer variables.